

Lecture 14

Michael Brodskiy

Professor: M. Onabajo

November 7, 2024

- Metal-Oxide Semiconductor Field-Effect Transistor (MOSFET)
 - Extremely high impedance looking into the gate
 - * $I_G \approx 0$
 - Body is often connected to the source or to ground (substrate)
 - Cutoff Region
 - * $V_{GS} < V_{to}$
 - V_{to} is the threshold voltage (technology-dependent parameter: .3[V] (new)
- 2[V] (older))
 - * $I_D = 0$
 - Triode Region
 - * $V_{GS} > V_{to}$ and $V_{DS} < V_{GS} - V_{to}$
 - * Also called “linear region”
 - $I_D \propto V_{GS}$ when V_{DS} is small
 - Voltage-controlled resistance (between drain and source terminals)
 - Saturation Region
 - * $V_{GS} > V_{to}$ and $V_{DS} > V_{GS} - V_{to}$
 - * $I_D = K(V_{GS} - V_{to})^2$ (desired mode for amplifiers)
 - Drain-Source Current:

$$I_D = \left(\frac{W}{L}\right) \left(\frac{KP}{2}\right) [2(V_{GS} - V_{to})V_{DS} - V_{DS}^2] [1 + \lambda V_{DS}]$$

- * Parameters:
 - L is the channel length, W is the channel width
 - $KP = \mu_n C_{ox} = \mu_n (\epsilon_{ox}/t_{ox})$
 - μ_n is the mobility of the electrons in the channel

- C_{ox} is the oxide capacitance per unit area
- $K = (W/L)(KP/2)$ has units of ampères per square volt
- λ is the channel length modulation parameter ($\lambda = 0$ in many hand-based calculation estimates)
- Boundary between triode and saturation regions:

$$I = \left(\frac{W}{L}\right) \left(\frac{KP}{2}\right) V_{DS}^2$$

- Small Signal Analysis with MOSFETS

- Hybrid- π small-signal model
 - * Parasitic capacitors are excluded here
 - The model is only valid at low and midband frequencies
- Parameters depend on the Q -point

$$g_m = \frac{2I_D}{V_{GSQ} - V_{to}} = KP \frac{W}{L} (V_{GSQ} - V_{to}) = \sqrt{2KP \frac{W}{L} I_D}$$

$$r_{ds} \approx \frac{1}{\lambda I_D} = \frac{|V_A|}{I_D}$$

- T-Model has the same structure, but with one addition:

$$r_{gs} = \frac{1}{g_m}$$

- MOSFETs in Triode Region

- Simple Triode-Region Model
 - * Parasitic capacitors are excluded here
 - The model is only valid at low and midband frequencies

$$r_{on} \approx \frac{1}{KP \frac{W}{L} (V_{GSQ} - V_{TH})}$$

- For AC signals with small amplitudes