

# Homework 5

Michael Brodskiy

Professor: M. Onabajo

October 22, 2024

1. (a) We may begin by writing:

$$N_A = 10^{16} \left[ \frac{1}{\text{cm}^3} \right] \quad \text{and} \quad N_D = 10^{18} \left[ \frac{1}{\text{cm}^3} \right]$$

We know that this silicon ( $N_A \neq N_D$ ) is  $n$ -type, so we may write the concentration of donors as:

$$n \approx N_D = 10^{18} \left[ \frac{1}{\text{cm}^3} \right]$$

From here, we use the mass action law to write:

$$np = n_i^2$$

Where  $n_i = 1.5 \cdot 10^{10} [\text{cm}^{-3}]$  for silicon at 300[K]. This gives us the hole concentration as:

$$p = \frac{(1.5 \cdot 10^{10})^2}{10^{18}}$$

$$p = 225 \left[ \frac{1}{\text{cm}^3} \right]$$

(b)

$$N_A = 10^{17} \left[ \frac{1}{\text{cm}^3} \right] \quad \text{and} \quad N_D = 10^{17} \left[ \frac{1}{\text{cm}^3} \right]$$

Given this, we know that this silicon is intrinsic like ( $N_A = N_D$ ). This means that we may write:

$$n + N_A = p + N_D$$

$$n + 10^{15} = p + 10^{15}$$

$$n = p$$

Using the mass-action law, we may write:

$$n = n_i$$

Which gives us:

$$n = p = 1.5 \cdot 10^{10} \left[ \frac{1}{\text{cm}^3} \right]$$

2. •  $V_{BE}$

We begin by using the transistor equation:

$$I_e = I_{ES} e^{\frac{V_{BE}}{V_T}}$$

This can be rearranged to get:

$$V_{BE} = V_T \ln \left( \frac{I_E}{I_{ES}} \right)$$

And now we enter known values:

$$V_{BE} = .026 \ln \left( \frac{.01}{10^{-13}} \right)$$

$$V_{BE} = .6585[\text{V}]$$

- $V_{BC}$

Since we are given  $V_{CE} > .2[\text{V}]$ , the BJT is active, and we can write:

$$V_{BC} = V_{BE} - V_{CE}$$

$$V_{BC} = .6585 - 10$$

$$V_{BC} = -9.3415[\text{V}]$$

- $I_B$

We may use the value of  $\beta$  to find:

$$I_B = (1 + \beta) I_E$$

$$I_B = (1 + 100)^{-1} (.01)$$

$$I_B = 99[\mu\text{A}]$$

- $I_C$

We then know:

$$I_C = \beta I_B$$

$$I_C = 100(99 \cdot 10^{-6})$$

$$\boxed{I_C = 9.9[\text{mA}]}$$

- $\alpha$

Finally, we find  $\alpha$ :

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\alpha = \frac{100}{100 + 1}$$

$$\boxed{\alpha = .9901}$$

3. •  $V_1$

Since there is a voltage drop from the base (due to forward-bias) to the emitter of  $.7[\text{V}]$ , we know:

$$\boxed{V_1 = -.7[\text{V}]}$$

- $V_2$

We may begin by finding the emitter current at transistor  $Q_1$ :

$$I_{EQ_1} = \frac{10 - .7}{4.7k}$$

$$I_{EQ_1} = 1.979[\text{mA}]$$

Given the  $\beta$  value, we may find the collector current as:

$$I_{CQ_1} = \frac{100}{101} I_{EQ_1}$$

$$I_{CQ_1} = 1.9594[\text{mA}]$$

We can then calculate  $V_2$  based on KVL:

$$V_2 = 10 - (1.9594)(5.1k)$$

$$\boxed{V_2 = 7.0297[\text{mV}]}$$

- $V_3$

Applying this voltage into a KVL equation for transistor  $Q_2$ , we may write:

$$I_{CQ_2} = \frac{10 - .0070297 - .7}{4.7k}$$

$$I_{CQ_2} = 1.9772[\text{mA}]$$

We can thus get  $V_3$  as:

$$V_3 = 10 - (1.9772)(4.7)$$

$$\boxed{V_3 = .707[\text{V}]}$$

- $V_4$

We then find the emitter voltage based on the  $\beta$ :

$$I_{EQ_2} = \frac{101}{100}(1.9772)$$

$$I_{EQ_2} = 1.997[\text{mA}]$$

Using KVL at the collector, we get:

$$V_4 = (3)(1.997) - 10$$

$$\boxed{V_4 = -4.0091[\text{V}]}$$

- $V_5$

We may find  $V_5$  using the voltage drop from a forward-biased diode:

$$V_5 = V_4 - .7$$

$$V_5 = -4.0091 - .7$$

$$\boxed{V_5 = -4.7091[\text{V}]}$$

- $V_6$

Using KVL at the input of  $Q_3$ , we get:

$$I_{EQ_3} = \frac{10 - 4.0091 - .7}{1.3k}$$

$$I_{EQ_3} = 4.0699[\text{mA}]$$

We then find the collector current:

$$I_{CQ_3} = \frac{\beta}{\beta + 1}(4.0699)$$

$$I_{CQ_3} = \frac{100}{101}(4.0699)$$

$$I_{CQ_3} = 4.0296[\text{mA}]$$

And, finally, we use KVL to get:

$$V_6 = 10 - (4.0296)(2)$$

$$\boxed{V_6 = 1.9408[\text{V}]}$$

We may demonstrate the values we found as:

$$V \left\{ \begin{array}{l} 1, \quad -.7 \\ 2, \quad 7.0297 \cdot 10^{-3} \\ 3, \quad .707 \\ 4, \quad -4.0091 \\ 5, \quad -4.7091 \\ 6, \quad 1.9408 \end{array} \right. [\text{V}]$$

4. First, we find the thermal voltage at  $180[^\circ\text{C}]$ :

$$V_{T_2} = \frac{(1.38 \cdot 10^{-23})(273 + 180)}{1.6 \cdot 10^{-19}}$$

$$V_{T_2} = .039071[\text{V}]$$

From here, we may write our temperature difference equation to determine the initial  $V_{BE}$  voltage at  $2[\text{mA}]$ :

$$V_{BE_o} = V_{BE_1} + .002(T_2 - T_1)$$

$$V_{BE_o} = -.7 + .002(150)$$

$$V_{BE_o} = -.4[\text{V}]$$

We then find the saturation current:

$$I_s = \frac{I_C}{e^{V_{BE_o}/V_{T_2}}}$$

$$I_s = \frac{.002}{e^{-.4/.039071}}$$

$$I_s = 71.585[\text{nA}]$$

Finally, from this we may write:

$$V_{BE_2} = (.039071) \ln \left( \frac{.0001}{71.585 \cdot 10^{-9}} \right)$$

$$\boxed{V_{BE_2} = .283[\text{V}]}$$

5. (a) From running the simulation, we obtain the following result:

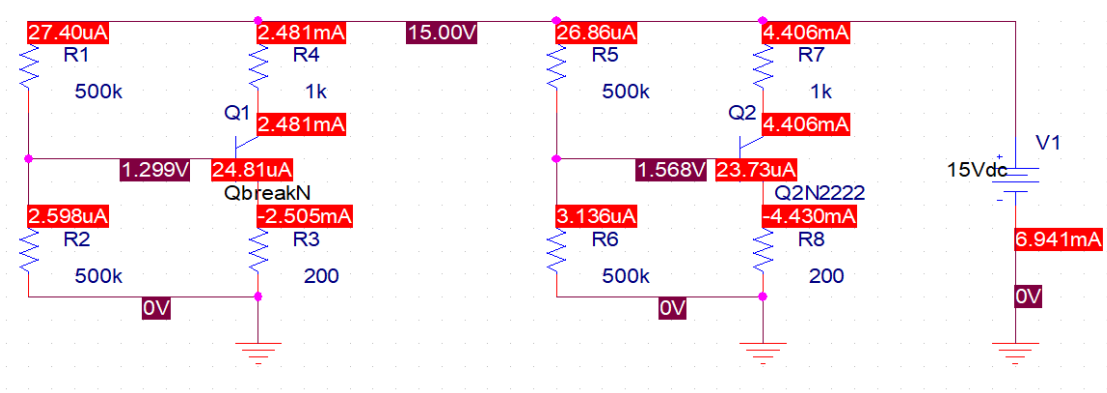


Figure 1: Simulation Results for Part (a)

From this, we may see that  $I_B = 23.73[\mu A]$  and  $I_C = 4.406[mA]$ . Thus, we may obtain:

$$\beta_{Q2} = \frac{4.406}{.02373}$$

$$\boxed{\beta_{Q2} = 185.67}$$

- (b) Once again, we simulate to obtain new values:

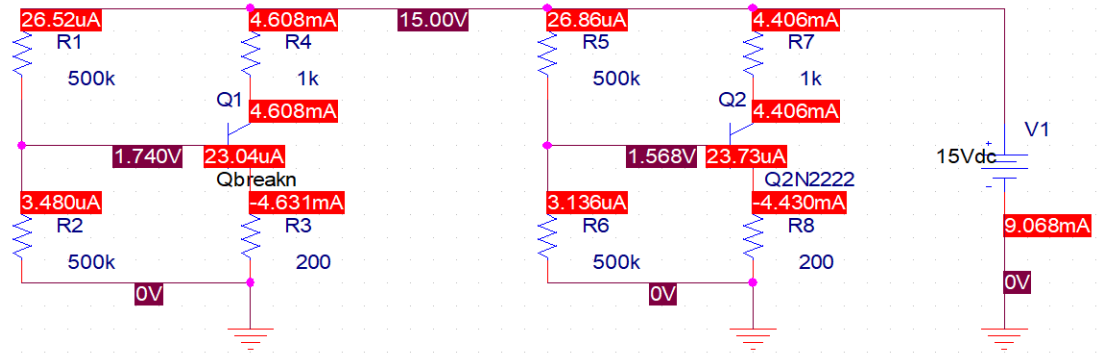


Figure 2: Simulation Results for Part (b)

Now, we get  $I_C = 4.608[mA]$  and  $I_B = 23.04[\mu A]$ , which gives us:

$$\beta_{QB} = \frac{4.608}{.02304}$$

$$\boxed{\beta_{QB} = 200}$$

This is the expected value, since we hard coded  $\beta$ .

(c) We may find the value of BF in the table below:

	Qbreakn	Q2N2222
	NPN	NPN
IS	100.000000E-18	14.340000E-15
BF	200	255.9
NF	1	1
VAF		74.03
IKF		.2847
ISE		14.340000E-15
NE		1.307
BR	1	6.092
NR	1	1
RB		10
RC		1
CJE		22.010000E-12
MJE		.377
CJC		7.306000E-12
MJC		.3416
TF		411.100000E-12
XTF		3
VTF		1.7
ITF		.6
TR		46.910000E-09
XTB		1.5
CN	2.42	2.42
D	.87	.87

Figure 3: Model Parameters

From this, we see that the expected BF value for the Q2N2222 is 255.9. Furthermore, we can confirm that BF for the other transistor is 200.

```

**** BIPOLAR JUNCTION TRANSISTORS

NAME      Q_Q1      Q_Q2
MODEL      Qbreakn  Q2N2222
IB         2.30E-05  2.37E-05
IC         4.61E-03  4.41E-03
VBE        8.14E-01  6.82E-01
VBC        -8.65E+00 -9.03E+00
VCE        9.47E+00  9.71E+00
BETADC     2.00E+02  1.86E+02
GM         1.78E-01  1.68E-01
RPI        1.12E+03  1.19E+03
RX         0.00E+00  1.00E+01
RO         1.00E+12  1.88E+04
CBE        0.00E+00  1.06E-10
CBC        0.00E+00  3.04E-12
CJS        0.00E+00  0.00E+00
BETAAC     2.00E+02  1.99E+02
CBX/CBX2   0.00E+00  0.00E+00
FT/FT2     2.84E+18  2.44E+08

```

Figure 4: Operating Point Parameters

Highlighted in the above figure, we see that BETADC is about 186 and BETAAC is about 199.

(d) The following data sheet was obtained online:



## ELECTRICAL CHARACTERISTICS

TC=25°C unless otherwise noted

Symbol	Ratings	Test Condition(s)		Min	Typ	Max	Unit
$V_{CE(SAT)}$	Collector-Emitter saturation Voltage (*)	$I_C=150\text{ mA}, I_B=15\text{ mA}$	2N2221-2N2222	-	-	0.4	V
			2N2221A-2N2222A	-	-	0.3	
		$I_C=500\text{ mA}, I_B=50\text{ mA}$	2N2221-2N2222	-	-	1.6	
			2N2221A-2N2222A	-	-	1	
$V_{BE(SAT)}$	Base-Emitter saturation Voltage (*)	$I_C=150\text{ mA}, I_B=15\text{ mA}$	2N2221-2N2222	-	-	1.3	V
			2N2221A-2N2222A	0.6	-	1.2	
		$I_C=500\text{ mA}, I_B=50\text{ mA}$	2N2221-2N2222	-	-	2.6	
			2N2221A-2N2222A	-	-	2	
$f_r$	Transition frequency	$I_C=20\text{ mA}, V_{CE}=20\text{ V}$ $f=100\text{ MHz}$	2N2221-2N22218A 2N2222	250	-	-	MHz
			2N2222A	300	-	-	
$h_{ie}$	Small signal current gain	$I_C=1\text{ mA}, V_{CE}=10\text{ V}$ $f=1\text{ kHz}$	2N2221A	30	-	150	-
			2N2222A	50	-	300	
		$I_C=10\text{ mA}, V_{CE}=10\text{ V}$ $f=1\text{ kHz}$	2N2221A	50	-	300	
			2N2222A	75	-	375	
$t_d$	Delay time	$I_C=150\text{ mA}, I_B=15\text{ mA}$ $-V_{BE}=0.5\text{ V}, V_{CC}=30\text{ V}$	2N2221A	-	-	10	ns
			2N2222A				
$t_r$	Rise time	$I_C=150\text{ mA}, I_B=15\text{ mA}$ $-V_{BE}=0.5\text{ V}, V_{CC}=30\text{ V}$	2N2221A	-	-	25	ns
			2N2222A				
$t_s$	Storage time	$I_C=150\text{ mA}, V_{CC}=30\text{ V}$ $I_{B1} = -I_{B2} = 15\text{ mA}$	2N2221A	-	-	225	ns
			2N2222A				
$t_f$	Fall time	$I_C=150\text{ mA}, V_{CC}=30\text{ V}$ $I_{B1} = -I_{B2} = 15\text{ mA}$	2N2221A	-	-	60	ns
			2N2222A				
$r_{b,Cc}$	Feedback time constant	$I_C=20\text{ mA}, V_{CE}=20\text{ V}$ $f=31.8\text{ MHz}$	2N2221A	-	-	150	ps
			2N2222A				

(\*) Pulse conditions :  $t_p < 300\text{ }\mu\text{s}$ ,  $\delta = 2\%$

Figure 5: Q2N2222 Sample Data Sheet

From the highlighted row, we may see that, for  $I_C = 1[\text{mA}]$  and  $V_{CE} = 10[\text{V}]$ , the current gain is between 50 and 300. Given that in our simulation  $I_C$  is just over 4 times as big, and  $V_{CE}$  is about 13.5[V], we can estimate that the value will be on the higher end of this range. As observed,  $\beta$  was 185.67, which is within the range specified by the data sheet.