

# Lecture 14

Michael Brodskiy

Professor: M. Onabajo

November 13, 2024

- Metal-Oxide Semiconductor Field-Effect Transistor (MOSFET)
  - Extremely high impedance looking into the gate
    - \*  $I_G \approx 0$
  - Body is often connected to the source or to ground (substrate)
  - Cutoff Region
    - \*  $V_{GS} < V_{to}$ 
      - $V_{to}$  is the threshold voltage (technology-dependent parameter: .3[V] (new)  
- 2[V] (older))
    - \*  $I_D = 0$
  - Triode Region
    - \*  $V_{GS} > V_{to}$  and  $V_{DS} < V_{GS} - V_{to}$
    - \* Also called “linear region”
      - $I_D \propto V_{GS}$  when  $V_{DS}$  is small
      - Voltage-controlled resistance (between drain and source terminals)
  - Saturation Region
    - \*  $V_{GS} > V_{to}$  and  $V_{DS} > V_{GS} - V_{to}$
    - \*  $I_D = K(V_{GS} - V_{to})^2$  (desired mode for amplifiers)
  - Drain-Source Current:

$$I_D = \left(\frac{W}{L}\right) \left(\frac{KP}{2}\right) [2(V_{GS} - V_{to})V_{DS} - V_{DS}^2] [1 + \lambda V_{DS}]$$

- \* Parameters:
  - $L$  is the channel length,  $W$  is the channel width
  - $KP = \mu_n C_{ox} = \mu_n (\epsilon_{ox}/t_{ox})$
  - $\mu_n$  is the mobility of the electrons in the channel

- $C_{ox}$  is the oxide capacitance per unit area
- $K = (W/L)(KP/2)$  has units of ampères per square volt
- $\lambda$  is the channel length modulation parameter ( $\lambda = 0$  in many hand-based calculation estimates)
- Boundary between triode and saturation regions:

$$I = \left(\frac{W}{L}\right) \left(\frac{KP}{2}\right) V_{DS}^2$$

- Small Signal Analysis with MOSFETS

- Hybrid- $\pi$  small-signal model
  - \* Parasitic capacitors are excluded here
    - The model is only valid at low and midband frequencies
- Parameters depend on the  $Q$ -point

$$g_m = \frac{2I_D}{V_{GSQ} - V_{to}} = KP \frac{W}{L} (V_{GSQ} - V_{to}) = \sqrt{2KP \frac{W}{L} I_D}$$

$$r_{ds} \approx \frac{1}{\lambda I_D} = \frac{|V_A|}{I_D}$$

- T-Model has the same structure, but with one addition:

$$r_{gs} = \frac{1}{g_m}$$

- MOSFETs in Triode Region

- Simple Triode-Region Model
  - \* Parasitic capacitors are excluded here
    - The model is only valid at low and midband frequencies

$$r_{on} \approx \frac{1}{KP \frac{W}{L} (V_{GSQ} - V_{TH})}$$

- For AC signals with small amplitudes

- Common-Source Amplifier Formulas

- Amplifier gain without load:

$$A_{vo} = \frac{v_o}{v_i} \approx -g_m(r_{ds} || R_D)$$

- Loaded voltage gain:

$$A_v = \frac{v_o}{v_i} \approx -g_m(r_{ds} || R_D || R_L)$$

- Gain from source to load:

$$A_{vs} = \frac{v_o}{v_{sig}} \approx -g_m \left[ \frac{R_i}{R_{sig} + R_i} \right] (r_{ds} || R_D || R_L)$$