

# Lecture 1

Michael Brodskiy

Professor: M. Onabajo

September 4 — September 5, 2024

- Broad circuit categories:
  - Information processing → cell phone, GPS, cable TV
  - Power delivery → AC-to-DC power adapter, power amplifiers, EVs
- Applications
  - Communication systems
  - Medical electronics
  - Computers (digital signal processing)
  - Instrumentation
  - Control systems
  - Power systems
  - Toys
- Electronic circuits that are manufactured as integrated circuits (ICs)
  - “Chips” — created with semiconductor device fabrication processes
- Semiconductor Industry
  - 1947
    - \* First transistor was invented at Bell Laboratories by William Shockley, John Bardeen, and Walter Brattain
    - \* “The basis of modern electronics”
  - 1958 — 1961
    - \* Introduction of the integrated circuit by Jack Kilby (Texas Instruments) and Robert Noyce (Fairchild Semiconductor)
    - \* Enabled miniaturization and mass production of chips

- Today
  - \* Smallest dimensions of features in the silicon around 5 [nm]
  - \* Up to >2.5 billion transistors per chip
  - \* >\$300 billion global revenue
- Course Overview
  - Amplifier concepts
  - Study of electronic devices
    - \* Operational amplifiers (Op-Amps)
    - \* Diodes
    - \* Bipolar junction transistors (BJTs)
    - \* Metal-oxide-semiconductor field effect transistors (MOSFETs)
  - Design and analysis of electronic circuits
    - \* Analog amplifiers, rectifier circuits
    - \* Digital logic
- Main Course Goals
  - Understand the operation of fundamental electronic devices (op-amps, diodes, BJTs, MOSFETs)
  - Analyze and design operational amplifier circuits and rectifier circuits
  - Analyze and design amplifiers with BJTs and MOSFETs
  - Be able to identify CMOS logic circuits (NOT, NAND, NOR), and analyze voltage transfer curves and propagation delays
  - Simulate electronic circuits using PSPICE
- Review — Some Circuit Analysis Highlights
  - Element combination rules (parallel, serial)
  - Ohm's Law:  $I = V/R$
  - KVL for a circuit loop  $\rightarrow \sum_j v_j = 0$
  - KCL at a node  $\rightarrow \sum_j i_j = 0$
  - Superposition principle
    - \* If input A produces response X and input B produces response Y, then input (A+B) produces response (X+Y)
    - \* Holds only for linear circuits
    - \* Very useful for circuits with multiple voltage and current sources
  - Thévenin and Norton form of signal sources

\* Valid only in linear circuits

- Element Combination Rules

- Resistors in series can be summed ( $R_1 + R_2 + \cdots + R_n = R_t$ )
- Resistors in parallel can be summed via conductances ( $G_x = \frac{1}{R_x}$ ) can be combined to get  $\rightarrow G_1 + G_2 + \cdots + G_n = G_t$
- Voltages in series can be summed ( $V_1 + V_2 + \cdots + V_n = V_t$ )
- Voltages in parallel will not occur, as it is illogical to place them in such a manner (and is the same reason current sources in series do not occur)
- Current sources in parallel may be summed ( $i_1 + i_2 + \cdots + i_n = i_t$ )

- Analysis of Large Circuits

- Write all expressions for the circuit
  - \* At elements (Ohm's Law)
  - \* At nodes (KCL)
  - \* For loops (KVL)
- Eliminate redundant equations (keep only independent equations)
- Solve the system of equations for the unknown variables

- Thévenin and Norton Equivalent Representations

- Thévenin to Norton transformation
  - \* Set  $I_s = V_s/R_s$  (short-circuit current), and  $R_P = R_s$
- Norton to Thévenin transformation
  - \* Set  $V_s = I_s R_s$  (open-circuit voltage), and  $R_s = R_P$
- In more complex cases,  $R_s$  and  $R_P$  are the equivalent resistances seen at terminals

- A circuit can be broken into “source” components by assuming an open circuit for current sources, and short circuit for voltage sources
- This gives us components which we can then sum up via the superposition principle:

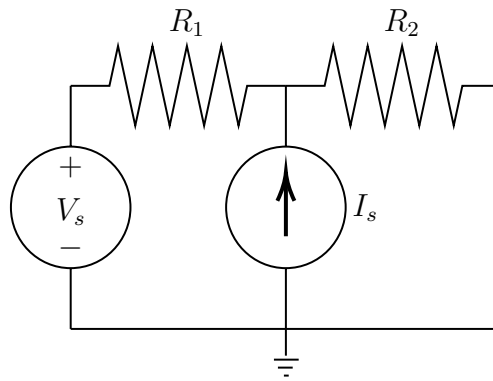


Figure 1: Initial Circuit

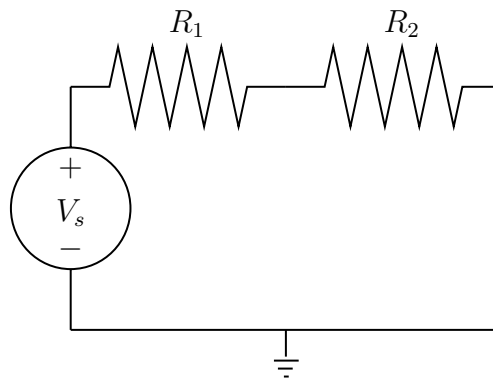


Figure 2: Voltage Component

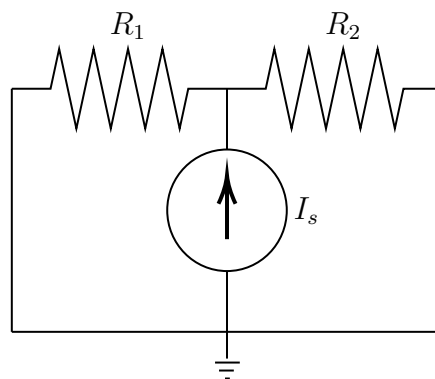


Figure 3: Current Component

- Amplification
  - Voltage gain:  $|A_v|$ 
    - \* When  $|A_v|$  is constant: linear amplifier
    - \* When  $|A_v|$  is not constant: non-linear amplifier
  - Non-inverting amplifier:  $v_o(t) = A_v v_i(t)$
  - Inverting amplifier:  $v_o(t) = -A_v v_i(t)$
- Voltage-Amplifier Model

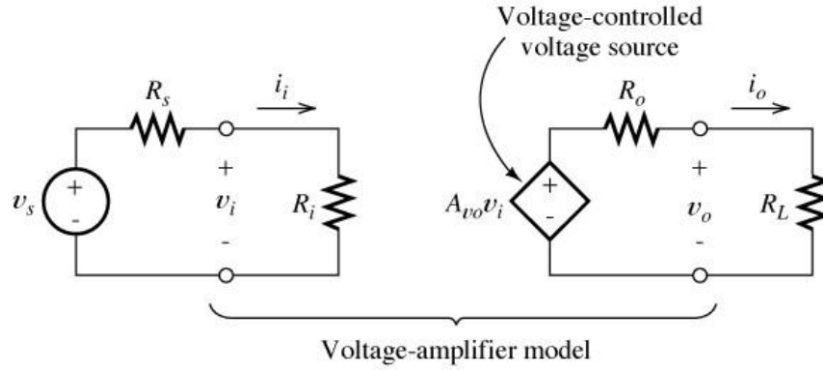


Figure 4: Reference Figure for the Voltage-Amplifier Model

- Parameters
  - \*  $v_s$  is the input voltage source, which has a series resistance  $R_s$
  - \*  $R_i$  and  $R_o$  are the input and output resistances, respectively
  - \*  $A_{vo}$  is the open-circuit voltage gain
  - \*  $R_L$  is the load resistance
- Remember: This is a simplified representation of an amplifier
- Current gain:  $A_i = \frac{i_o}{i_i} = \frac{(v_o/R_L)}{(v_i/R_i)} = A_v(R_i/R_L)$
- Loaded voltage gain:  $A_v = \frac{v_o}{v_i} \neq A_{vo}$
- Power gain:  $G = \frac{P_o}{P_i} = \frac{V_o I_o}{\underbrace{V_i I_i}_{\text{RMS}}} = A_v A_i = A_v^2 \cdot \frac{R_i}{R_L}$
- For optimum voltage transfer,  $R_L \gg R_o$
- Loading Effects
  - Refer to the same figure (Figure 4) as for the Voltage-Amplifier Mode

- Input signal attenuation:  $v_i = v_s \left( \frac{R_i}{R_i + R_s} \right)$
- Output signal attenuation:  $v_o = A_{vo} v_i \left( \frac{R_L}{R_L + R_o} \right)$
- Loaded voltage gain of the amplifier:  $A_v = \frac{v_o}{v_i} = A_{vo} \left( \frac{R_L}{R_L + R_o} \right)$
- Voltage gain from source to load  $A_{vs} = \frac{v_o}{v_s} = A_{vo} \left( \frac{R_i}{R_i + R_s} \right) \left( \frac{R_L}{R_L + R_o} \right)$

- Decibel Notation

- Use  $20 \log(X)$  for voltages and currents
  - \*  $A_{v\text{dB}} = 20 \log(|A_v|)$
  - \*  $A_{i\text{dB}} = 20 \log(|A_i|)$
- Use  $10 \log(X)$  for powers
  - \*  $G_{\text{dB}} = 10 \log(|G|)$
- Quantities in decibels are added when two or more amplifiers are connected in series (called “cascaded”)