

# Lecture 3

Michael Brodskiy

Professor: M. Onabajo

September 11, 2024

- Frequency Dependence (Impedance)

- Capacitor

$$Z_c = \frac{1}{j\omega C}$$

- Inductors

$$Z_L = j\omega L = SL$$

- Note, for capacitors impedance decreases with frequency, while it increases with frequency for inductors

- DC Coupling

- Amplifier stages are directly connected together
- High-frequency gain decreases (“rolls off”) due to unwanted (“parasitic”) capacitances and inductances

- AC Coupling

- Input-coupling capacitors are sometimes referred to as DC-blocking Capacitors
- Improved isolation between stages because the capacitors “block” DC current/voltages ( $Z_c = 1/j\omega C \rightarrow \text{infinite impedance at } \omega = 0$ )
- Impacts the low-frequency response

- Impact of Parasitics (Stray Inductances/Capacitances)

- Stray inductances/capacitances (often called “parasitics”) result from non-ideal properties of materials:
  - \* Integrated circuits, chip packages, printed circuit boards, cables, ...

- High-frequency gain reduction from:
  - \* Capacitors in parallel with the signal path
  - \* Inductors in series with the signal path
- Computer-based simulations are used for complex models and circuits
- Half-Power Bandwidth
  - $P_o = (AV_{\text{inRMS}})^2/R_L \rightarrow P_o = P_{\text{max}}/2$  when  $A = A_{\text{max}}/\sqrt{2}$
  - By convention, the frequencies  $f_H$  and  $f_L$  at which  $P_o = P_{\text{max}}/2$  are referred to as half-power frequencies or  $-3\text{dB}$  frequencies
    - \* Note:  $20 \log(A_{\text{max}}/\sqrt{2}) = 20 \log(A_{\text{max}}) - 20 \log(\sqrt{2}) = A_{\text{max(dB)}} - 3.01\text{dB}$
  - Amplifier bandwidth:  $B = f_H - f_L$
- Complex Gain, Frequency Response
  - Complex transfer function  $T(j\omega)$ 
    - \*  $s = j\omega = j(2\pi f) \rightarrow T(s) = \frac{V_o(s)}{V_i(s)}$
    - \* Frequency-dependent gain and phase
    - \*  $|T|\angle\phi = R + jX$ , where  $|T| = (R^2 + X^2)^{1/2}$ ,  $\phi = \tan^{-1}(\frac{X}{R})$
- First-Order Low-Pass Filter
  - $V_o(s) = V_i(s) \frac{Z_c}{Z_c + Z_r}$ , where  $Z_r = R$ ,  $Z_c = \frac{1}{sC} = \frac{1}{j\omega C}$
  - $T(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1/(j\omega C)}{(1/j\omega C) + R} = \frac{1}{1 + j\omega RC}$
  - Let  $\omega_o = (1/RC) = (1/\tau)$  and  $K = 1$ 
    - \*  $\tau = RC$  is the only time constant of this circuit with a single pole formed by the resistor and capacitor
    - \*  $T(j\omega) = \frac{K}{[1 + j\frac{\omega}{\omega_o}]}$
- Transfer Function Normalization (First-Order LPF Case)
  - Typically,  $K \neq 1$
  - When normalizing a magnitude response, plot:  $|T(j\omega)/K|$ 
    - \*  $20 \log(|T(j\omega)/K|) = 20 \log(1) = 0[\text{dB}]$  becomes max gain
  - Low-pass filter characteristics:
    - \* For  $\omega \ll \omega_o$ :  $|T(j\omega)/K| \approx 1$  ( $0[\text{dB}]$ )
    - \* For  $\omega \gg \omega_o$ :  $|T(j\omega)/K| \approx \frac{\omega_o}{\omega} \rightarrow$  high-frequency roll-off

- \* Slope is -20[dB]/decade (or -6[dB]/octave)

- Bode Plot of the Low-Pass Filter

- Attenuates high-frequency signal components
- “Corner frequency”  $\leftrightarrow$  -3[dB] frequency is the “cutoff frequency”
  - \* Often labeled  $f_c(\omega_c)$ ,  $f_{3dB}$ ,  $(\omega_{3dB})$ ,  $f_o(\omega_o)$ , or  $f_B(\omega_B)$
  - \* In the LPF case, the corner frequency is often called “bandwidth of the filter”

- First-Order High Pass Filter

$$T(j\omega) = \frac{1}{1 - j(\omega_o/\omega)}$$

- Where  $\omega_o = 1/(RC) = (1/\tau)$ , with  $\tau = RC$  as the time constant
- In general:

$$T(j\omega) = \frac{K}{1 - j(\omega_o/\omega)}$$

- \* As  $\omega \rightarrow 0$ ,  $T(j\omega \rightarrow 0)$  (low frequency rejection)
- \* As  $\omega \rightarrow \infty$ ,  $T(j\omega \rightarrow \infty) = K$  (high frequency transmission)

- Bode Plot of the High-Pass Filter

- Attenuates low-frequency components
- “Corner frequency”  $\leftrightarrow$  -3[dB] frequency is the “cutoff frequency”
  - \* Often labeled  $f_c(\omega_c)$ ,  $f_{3dB}$ ,  $(\omega_{3dB})$
  - \*  $f_{3dB} \neq$  bandwidth

- Bandpass (Mid-Band) Filter

- Attenuates signal components outside of bandwidth
- Bandwidth:  $B = f_{c(LP)} - f_{c(HP)} = f_{\text{High3dB}} - f_{\text{Low3dB}}$

- Ideal Operational Amplifiers (Op-Amps)

- Infinite open-loop differential gain  $A_{dOL} = V_o/(V_+ - V_-)$
- Infinite input impedance ( $R_i = \infty$ ,  $i_{in+} = i_{in-} = 0$ )
- Zero output impedance ( $R_o = 0$ )
- Zero common-mode gain (CMRR= $A_{dOL}/A_{cm} = \infty$ )
- Infinite bandwidth (no high or low frequency gain roll-off)

- The Summing-Point Constraint
  - Only applies when the op-amp is used in negative feedback, which is often the case
  - Assuming the ideal op-amp (in particular:  $A_{dOL} = \infty$ ), the feedback action forces  $V_+ - V_- = 0$  (a virtual short-circuit between the terminals)
    - \* No current flow into the input terminals