

Homework 10

Michael Brodskiy

Professor: M. Onabajo

November 7, 2024

- 1.
2. First, we know that $I_G = 0$ since the input impedance of the MOSFET is high. In this manner, we may write:

$$I_{DQ} = I_{SQ}$$

Using KVL, we may obtain:

$$V_{DD} = V_{GS} + I_{DQ}R_S$$

$$V_{GS} = 15 - 3000I_{DQ}$$

Assuming the MOSFET is operating in the saturated region, we may write:

$$I_{DQ} = K(V_{GS} - V_{to})^2$$

$$I_{DQ} = .25(15 - 3000I_{DQ} - 1)^2$$

$$I_{DQ} = .25(14 - 3000I_{DQ})^2$$

$$I_{DQ} = 2250I_{DQ}^2 - 21I_{DQ} + .049$$

$$0 = 2250I_{DQ}^2 - 22I_{DQ} + .049$$

Solving the equation, we obtain:

$$I_{DQ} = 4.889 \cdot 10^{-3} \pm 1.4572 \cdot 10^{-4}$$

$$I_{DQ} = 6.3461, 3.4317[\text{mA}]$$

We now check the voltage in both cases. Let us use the first value to find the gate-to-source voltage:

$$V_{GS1} = 15 - (3000)(I_{DQ})$$

$$V_{GS1} = 15 - (3)(6.3461)$$

$$\boxed{V_{GS1} = -4.0383[\text{V}]}$$

We may observe that, in this case, the transistor is off. Now, we use the second value:

$$V_{GS2} = 15 - (3000)(I_{DQ})$$

$$V_{GS2} = 15 - (3)(3.4317)$$

$$\boxed{V_{GS2} = 4.7049[\text{V}]}$$

We see that the transistor is on only for the second value. Thus, we proceed with the second drain current value. This gives us:

$$V_{DD} - I_{DQ}(R_D) - V_{DSQ} - I_{DQ}(R_S) + V_{DD} = 0$$

$$30 - I_{DQ}(R_D) - I_{DQ}(R_S) = V_{DSQ}$$

We can solve using our known values:

$$V_{DSQ} = 30 - 3.4317(4)$$

$$\boxed{V_{DSQ} = 16.273[\text{V}]}$$

We may observe that both $V_{GS} > V_{to}$ and $V_{DSQ} \geq V_{GS} - V_{to}$ are true, meaning that our saturation assumption was valid. As such, we have found our values for the given transistor.

3.