

Lecture 8

Michael Brodskiy

Professor: M. Onabajo

September 30, 2024

- PN-Junction Diodes

- Shockley Equation (“Diode Equation”)

- * More realistic model for the I-V characteristics (for FB and RB regions)
 - * Based on semiconductor physics

$$i_D = I_s e^{V_D/(nV_T)} + 1$$

- I_s is the saturation current (10^{-6} to 10^{-18} [A])

- n = diode ideality factor, also called emissions coefficient, and can range from 1 to 2

- $V_T = (kT)/q$ is the thermal voltage (≈ 26 [mV] at $T = 300$ [K] room temperature)

- * k = Boltzmann’s constant ($1.38 \cdot 10^{-23}$ [J/K]), q = electron charge ($1.6 \cdot 10^{-19}$ [C])

- Temperature Dependence

- At a constant current, the voltage drop decreases approximately 2[mV] for every 1[°C] increase in temperature

- Solving Circuits using the Junction Diode Model

- Iterative Approach

- * Pro: accurate hand calculations
 - * Con: tedious (time-consuming)

- Graphical Approach

- * Pro: fast
 - * Con: inaccurate (unless done numerically with a computer program)

- Simulation

- * Pro: most accurate
- * Con: limited insights into the trade-offs
- Constant Voltage Drop (CVD) Model
 - Diode approximation with an open-circuit (RB) or with a DC voltage source of V_{dc} ($\approx .7[V]$) to model the forward voltage drop (FB)
 - With the Resistance Model
 - * The diode is modeled with an open-circuit (RB), or with a DC voltage source and series resistance (FB), where $V_{do} \approx .7[V]$
 - * Dynamic resistance: $r_d = (nV_T)/I_{DQ}$
 - Approximated around the operating point Q (quiescent point)
 - A small-signal parameter (represents the diode's resistance associated with small changes of i_d and V_d)
- Zener Diode Modeling
 - Forward Bias (FB): $I_D > 0$
 - Reverse Bias (RB): $-V_{zo} < V_d < V_{do}$
 - Breakdown (BD): $I_z = -I_D > 0$, $V_D = -V_{zo} - I_z r_z$
 - Voltage Regulation:
 - * Voltage regulator quality indicators:
 - Source regulation: $\frac{\Delta V_{load}}{\Delta V_{SS}} \cdot 100\%$
 - Load regulation: $\frac{V_{NOload} - V_{FULLload}}{V_{FULLload}} \cdot 100\%$