

Homework 4

Michael Brodskiy

Professor: M. Onabajo

October 5, 2024

1. (a) Let us assume the diode is in forward bias. In this case, the circuit consists simply of the source and resistor, which gives us current:

$$I = \frac{v_{in}}{R}$$

Given that this value is sinusoidal, when greater than zero, we know that our initial assumption was true. When the voltage is zero or negative, the ideal diode is reverse-biased. We can now proceed to say:

$$v_o = \begin{cases} v_{in}, & v_{in} > 0 \\ 0, & v_{in} \leq 0 \end{cases}$$

Given that the given equation is:

$$v_{in} = 10 \sin(200\pi t)$$

we know that v_{in} is positive when $2n\pi \leq 200\pi t \leq (2n+1)\pi$, with $n = 0, 1, 2, \dots$. This gives: $(n/100) \leq t \leq (2n+1)/200$, which we can use to plot the transfer function (v_o/v_{in}):

$$H(t) = \frac{v_o}{v_{in}} = \begin{cases} 1, & (n/100) \leq t \leq (2n+1)/200 \\ 0, & \text{otherwise} \end{cases}$$

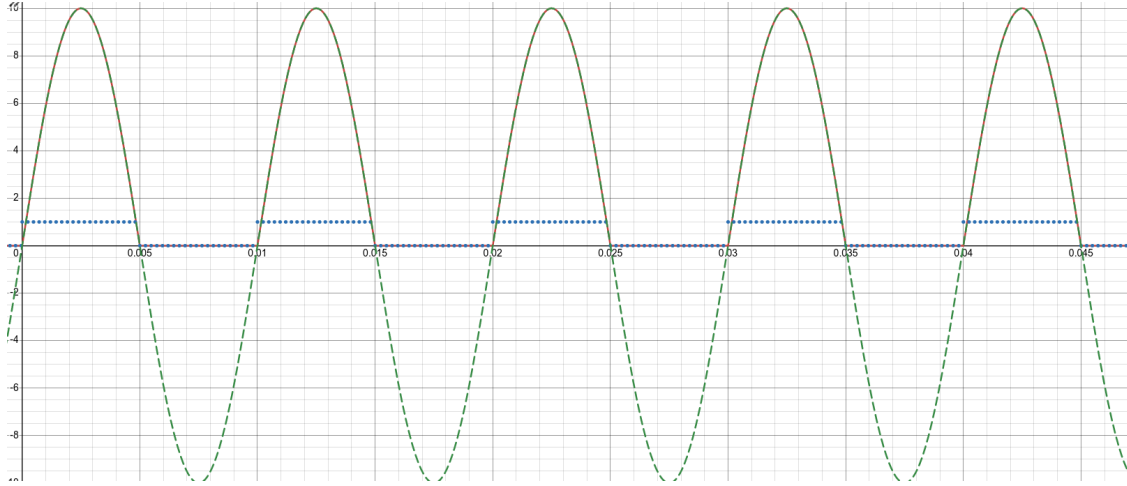


Figure 1: $H(t)$ (blue), v_{in} (green), and v_o (red) in Time Domain

Plotting v_o versus v_{in} , we find a linear relationship:

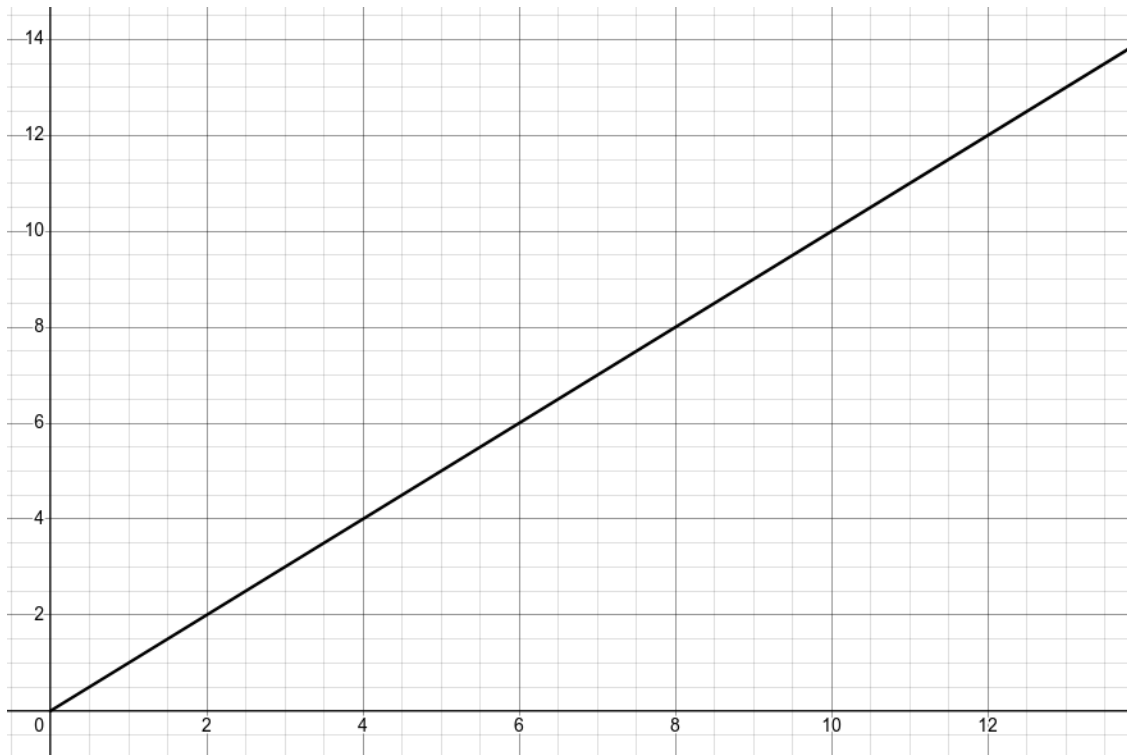


Figure 2: v_o versus v_{in} (1:1 relationship)

- (b) Similar to part (a), let us assume this diode is forward biased. In this case, we have the same current flow, indicating that this assumption is correct; however, the cycle is reversed in that v_o is zero when the diode is forward-biased, and $v_o = v_{in}$ when it is reverse biased. Thus, we may write this as:

$$v_o = \begin{cases} v_{in}, & v_{in} \leq 0 \\ 0, & v_{in} > 0 \end{cases}$$

$$H(t) = \frac{v_o}{v_{in}} = \begin{cases} 0, & (n/100) \leq t \leq (2n+1)/200 \\ 1, & \text{otherwise} \end{cases}$$

This gives us the following plot:

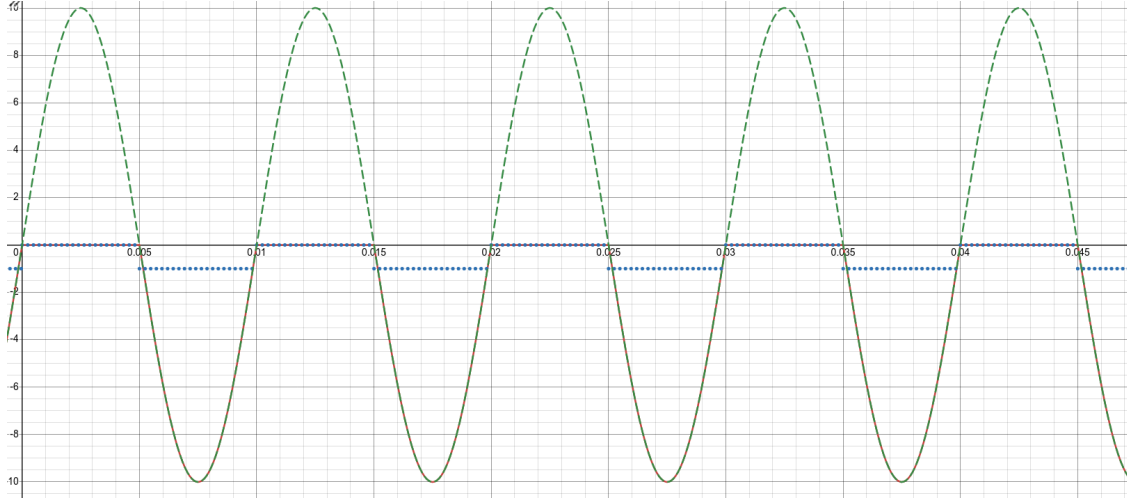


Figure 3: $H(t)$ (blue), v_{in} (green), and v_o (red) in Time Domain

Plotting v_o versus v_{in} , we find a linear relationship:

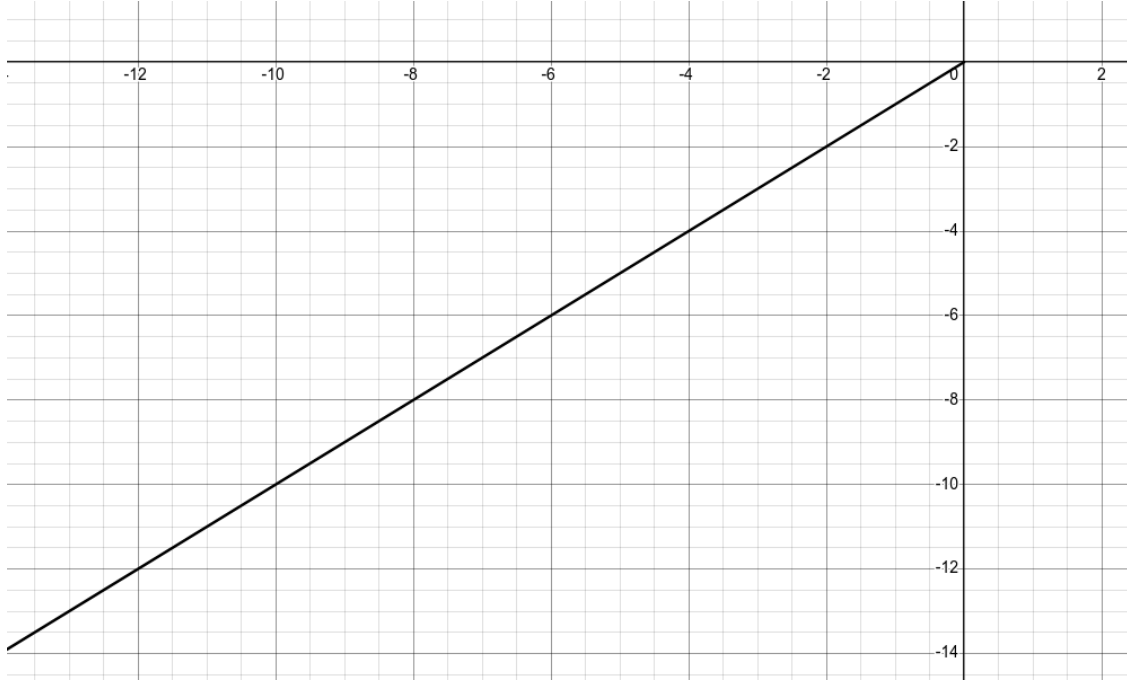


Figure 4: v_o versus v_{in} (1:-1 relationship)

- (c) Using a non-ideal, constant voltage drop (CVD) model, we know that, since there is one diode in each circuit, the output will be $.7[V]$ less for a forward-biased diode. For circuit 1, this gives us:

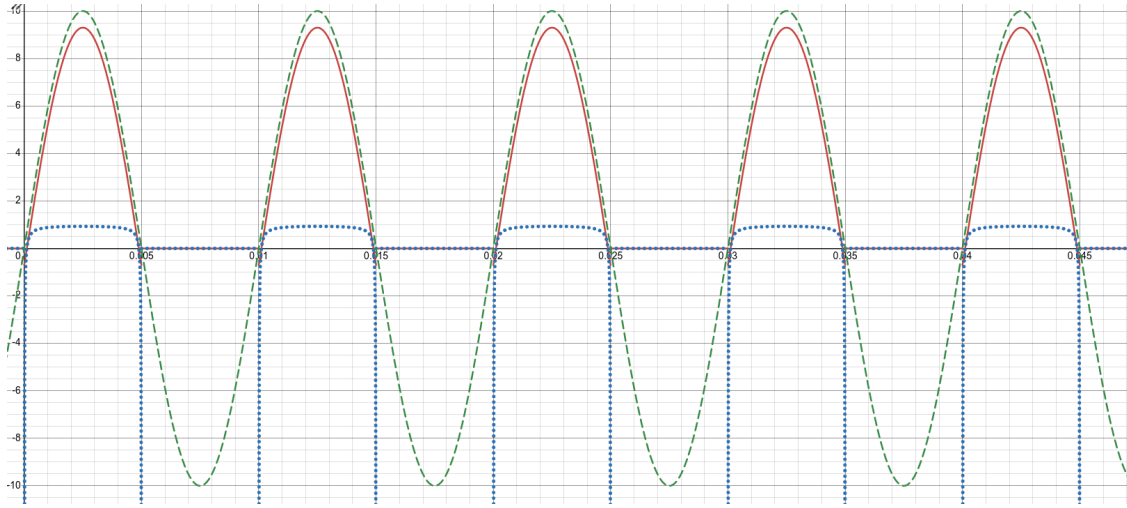


Figure 5: $H(t)$ (blue), v_{in} (green), and v_o (red) in Time Domain

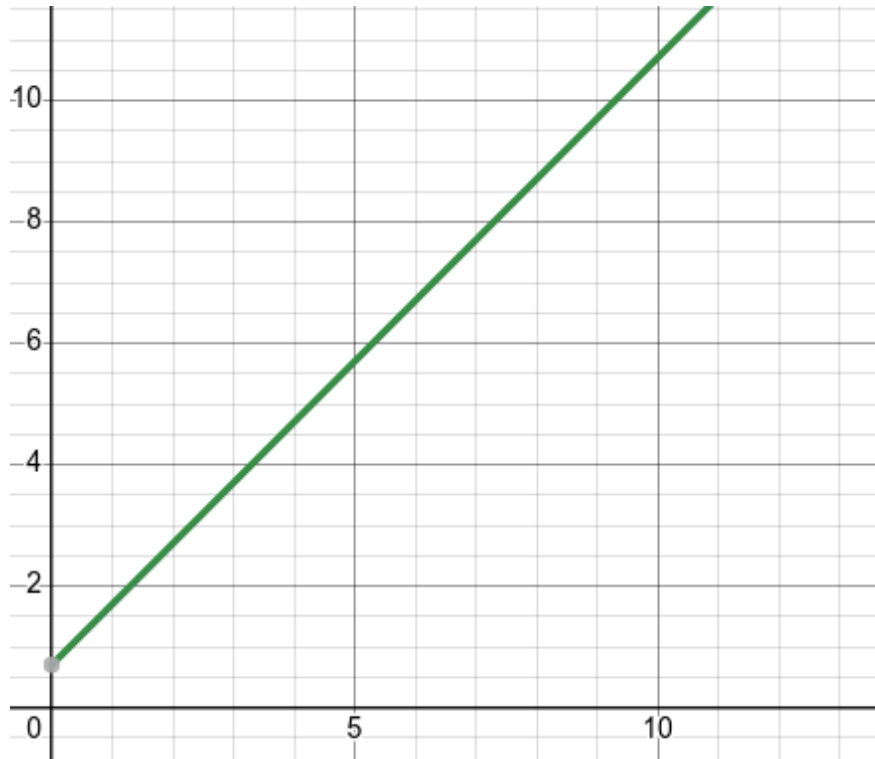


Figure 6: v_o versus v_{in}

Since the voltage was, initially, just zero when the diode was forward-biased (in the ideal case), with CVD we get:

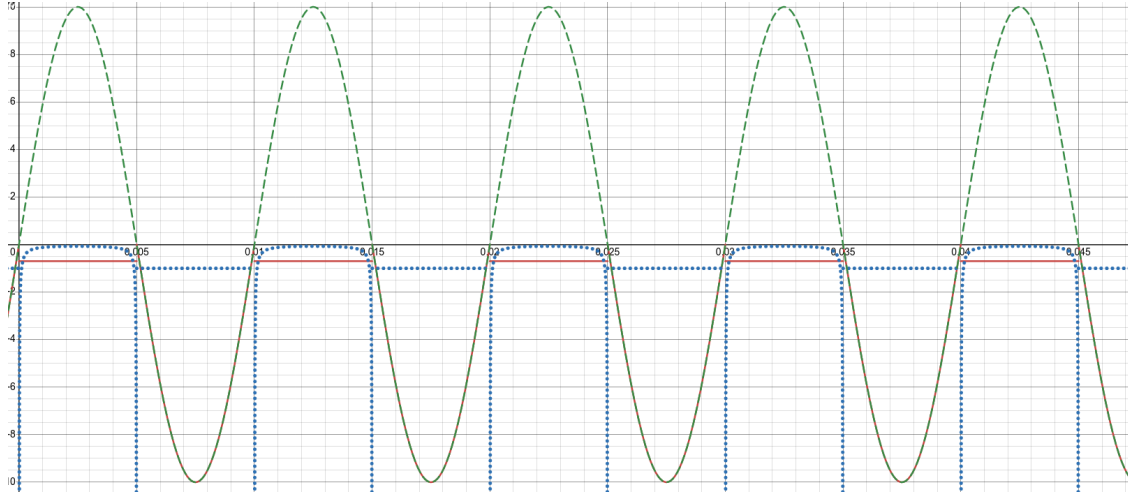


Figure 7: $H(t)$ (blue), v_{in} (green), and v_o (red) in Time Domain

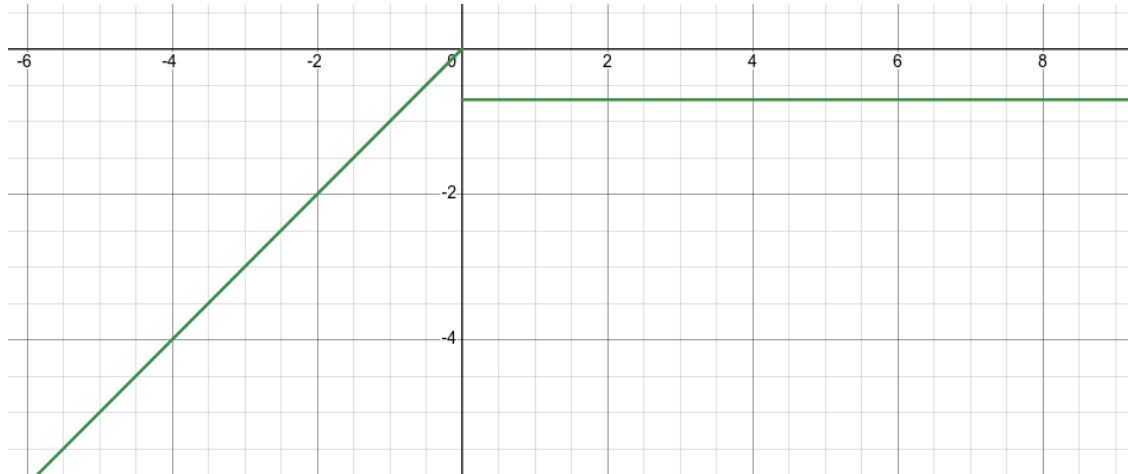


Figure 8: $H(t)$ (blue), v_{in} (green), and v_o (red) in Time Domain

2. (a) We begin by finding the maximum voltage value of the rectifier. Since we know the peak-to-peak ripple, we find the extrema:

$$V_{ext} = V_{avg} \pm \frac{V_{pp}}{2}$$

$$V_{ext} = 9 \pm 1$$

Thus, we see the minimum load voltage is 8[V], with:

$$V_{max} = 10[V]$$

- (b) We know that the peak secondary voltage must be 10[V]. Given this, we can write the turns ratio as (note we need to convert to RMS value):

$$n = \frac{N_1}{N_2} = \frac{V_1}{V_2}$$

$$n = \frac{220}{10\sqrt{2}}$$

$$\boxed{n = 15.6}$$

(c) We can write the equation for capacitance as:

$$C = \frac{I_L T}{V_r}$$

$$C = \frac{(.1)(.01667)}{2}$$

$$\boxed{C = .833[\text{mF}]}$$

We can now construct the circuit and get:

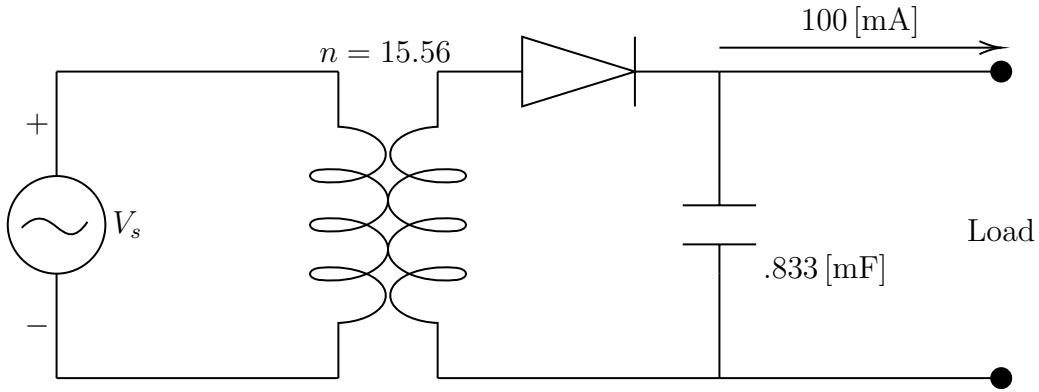


Figure 9: Half-Wave Rectifier Circuit, $V_{max} = 10[\text{V}]$

3. (a) We can see that, if the diode is forward-biased, the current through D can be found as (since the AC source can be omitted in the CVD model):

$$I_D = \frac{7 - .7}{5k}$$

$$\boxed{I_D = 1.26[\text{mA}]}$$

The output voltage is simply the drop across the diode, or:

$$\boxed{V_D = .7[\text{V}]}$$

Since the sinusoid can not exceed $-1[\text{V}]$, we see that the current is always positive, and, therefore, D is always forward-biased.

(b) We may write the Shockley equation as:

$$I_D = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

Using the given values, we obtain:

$$I_D = 10^{-14} \left(e^{\frac{V_D}{(.025)}} - 1 \right)$$

Using I_D from part (a), we get:

$$(2 \cdot 10^{10}) (6.3) + 1 = e^{40V_D}$$

$$V_D = \ln[(2 \cdot 10^{10}) (6.3) + 1]$$

$$\boxed{V_D = .639[\text{V}]}$$

(c) The dynamic resistance formula may be written as:

$$r_d = \frac{nV_T}{I_D}$$

Which gets us:

$$r_d = \frac{(.025)}{1.26 \cdot 10^{-3}}$$

$$\boxed{r_d = 19.841[\Omega]}$$

This means that, in the small-signal model, the diode acts as a resistor, which means we have a voltage divider. We can find the AC voltage across the diode using:

$$V_{ac} = (7 - .7 + V_s) \frac{19.841}{19.841 + 5000}$$

$$V_{ac} = (.02445 + .0039525 \sin(120\pi t))$$

This gets us:

$$\boxed{V_{ac} = .02445 + .0039525 \sin(120\pi t)[\text{V}]}$$

Summing the AC and DC components (the DC value would be from the CVD model), we get:

$$\boxed{V_D = .72445 + (3.953 \cdot 10^{-3}) \sin(120\pi t)[\text{V}]}$$

4. We may begin by analyzing the circuit response to various values of V_s . Let us begin with the case when $V_s = 0$. Here, D_1 would form an open circuit, which lets us calculate the current:

$$I = \frac{5 - .7}{6k}$$

$$I = .7167[\text{mA}]$$

Thus, we can find V_o :

$$V_o = 5 - 5k(I)$$

$$V_o = 1.4167[\text{V}]$$

Here, let us call the node above the single kilo-ohm resistor and ground as V_n . We know that, when $V_s - .7 < V_x$, D_1 remains off, while D_2 is on, so the response remains the same as above (note: $V_x = .7167[\text{V}]$ when D_1 is off); however, let us test $V_s - .7 \geq V_n$. In this case, D_2 is on until $V_n < 4.3[\text{V}]$, or $V_s < 5[\text{V}]$, at which point we can see:

$$V_o = V_s$$

In the case that $V_s \geq 5[\text{V}]$, D_2 shuts off, and the output is simply $5[\text{V}]$. Now that we have the pieces, we may plot the entire transfer function:

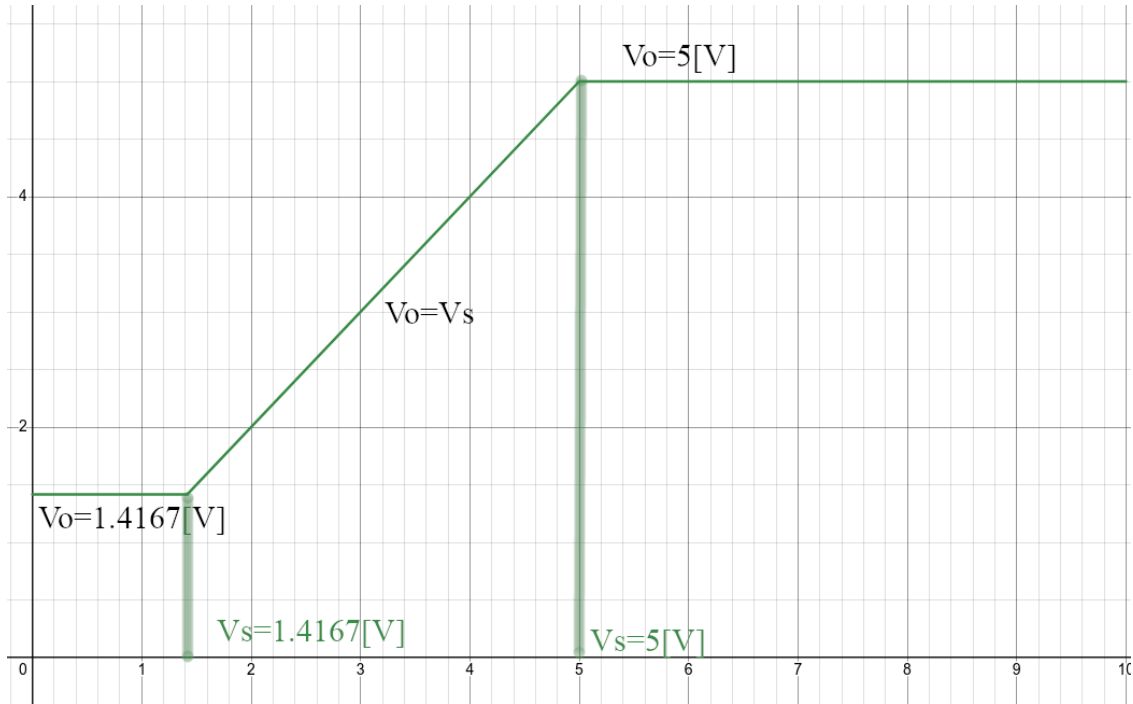


Figure 10: Transfer Characteristics of Given Circuit

5. We begin by generating the schematic:

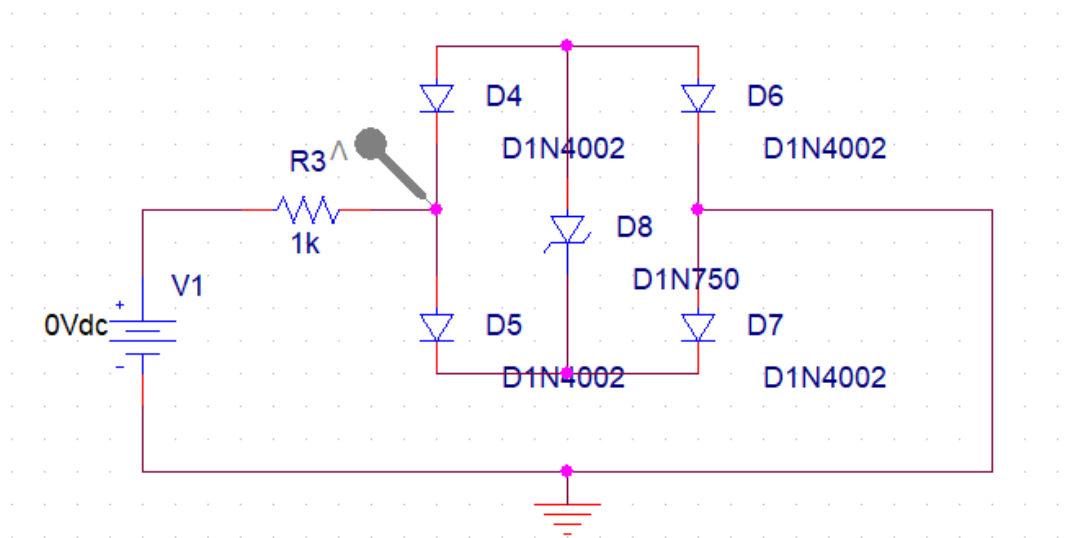


Figure 11: Schematic for DC Sweep

From here, we can simulate with the range $-15 \leq V_{in} \leq 15$:

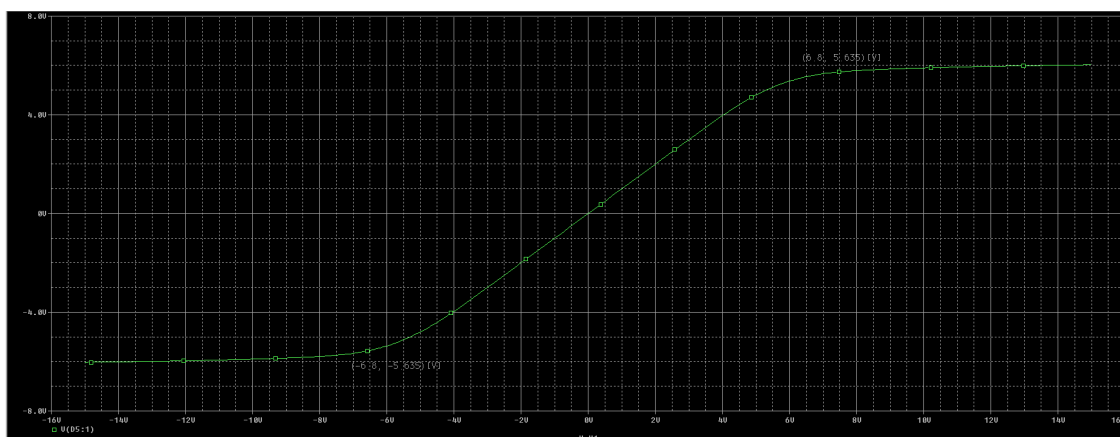


Figure 12: DC Sweep Transfer Characteristics

With the sweep, we may see that the maximum voltage magnitude is approximately 6[V], as expected for the circuit. Furthermore, the knee values occur at, approximately, the voltage value of the zener diode, or $V_z = 6.8[V]$. We can test the same circuit with an AC input:

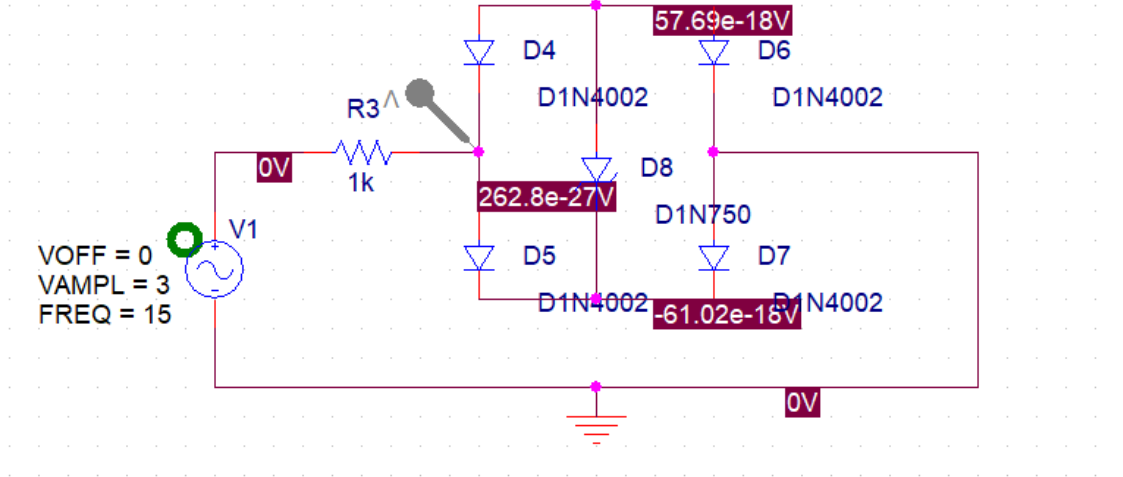


Figure 13: Schematic for AC Sweep

Using this circuit, we obtain the results for a wave with magnitude 3[V] and 12[V]:



Figure 14: Transfer Characteristics for 3[V] Amplitude Input



Figure 15: Transfer Characteristics for 12[V] Amplitude Input

We may note that, for the 3[V] amplitude, the transfer characteristics are a perfect line, with a slope of 1. This is due to the fact that $\pm 3[\text{V}]$ is within the permitted voltage range of the diodes; however, the 12[V] amplitude exceeds the $\pm 6[\text{V}]$ input range. This causes the curve to become 'S' shaped, where it tapers off as the magnitudes approach 6[V]. Furthermore, note that the knee values occur at the same points, indicating that, for diodes, only the magnitude, and not frequency, of the input make a difference.