

Lecture 9

Michael Brodskiy

Professor: M. Onabajo

October 3, 2024

- Rectifiers

- Simple Half-Wave Rectifiers

- * Used for AC-to-DC conversion
 - * Circuit representation when the diode is forward biased
 - $V_o = V_i$
 - $I_D = V_o/R_L$
 - * Average output voltage: $V_{oAVG} = V_{oPK}/\pi$
 - * RMS output voltage: $V_{oRMS} = V_{oPK}/2$

- Half-Wave Rectifier with Smoothing Capacitor

- * Addition of a capacitor in parallel with the load resistor
 - Formation of a first-order low-pass filter
 - Impedance of R_L and C in parallel

$$Z_P = \frac{1}{(1/R_L) + sC} = \frac{R_L}{1 + j(\omega/\omega_B)}, \quad \text{where } \omega_B = (1/RC)$$

- * The capacitor charges to V_i when the diode is on ($I_D = I_C + I_L$)
 - $I_C > 0$ when $V_o = V_c < V_i$, $I_C = 0$ when $V_o = V_c = V_i$ (ideal model)
 - * The capacitor holds (stores the output voltage when the diode is off)
 - V_o reduces gradually due to discharge of the capacitor: $I_C = -I_L$
 - * Average output voltage: $V_{oAVG} \approx V_{iPK} - (V_r/2)$
 - V_r is the ripple voltage (design starting point: only for the half-wave rectifier)
 - Goal for a given input signal period (T): minimum $V_r \rightarrow$ maximum V_o

- Electrostatic Discharge (ESD) Protection

- ESD event

- * Rapid discharge of charge between two bodies at different potentials
 - * High voltage build-up \rightarrow current flow (can destroy internal circuits)
 - * Occurs during the manufacturing and lifetime of a chip (pins come into contact with equipment and sometimes people)
- Simplified ESD protection concept with diodes
- Transformers
 - Convert voltage based on a turns ratio, $N_p : N_s$, or simplified $n : 1$, where:

$$V_s = \frac{V_p}{n}$$
- Full-Wave Rectifiers
 - Begins with a transformer, which isolates AC input to bridge from ground
 - Proceeds to a square arrangement of diodes, with one node grounded (current path for positive half-cycle)
 - Proceeds to a load resistance connected to ground