

Homework 8/9  
Fundamentals of Electronics  
EECE2412/3

Michael BRODSKIY  
Brodskiy.M@Northeastern.edu

November 21, 2024

Instructor: Professor ONABAJO

### **Abstract**

The purpose of this document is to outline the design process for a common-emitter bipolar junction transistor (BJT) amplifier with specified characteristics. The design process involved creating a viable circuit, calculating expected results, and simulating to confirm expectations.

KEYWORDS: common-emitter, BJT, amplifier

## Contents

<b>1</b>	<b>Introduction</b>	<b>4</b>
<b>2</b>	<b>Circuit Design</b>	<b>4</b>
2.1	Given Parameters . . . . .	5
2.2	DC Analysis . . . . .	5
2.2.1	Worst-Case Assumption . . . . .	6
2.2.2	Finding Applicable $R_B$ and $R_C$ Values . . . . .	6
2.3	Small-Signal Analysis . . . . .	6
2.3.1	Input Impedance Calculation . . . . .	7
2.3.2	Gain Calculation . . . . .	8
2.3.3	Output Impedance Calculation . . . . .	9
<b>3</b>	<b>Simulation</b>	<b>10</b>
3.1	Bias Point Performance . . . . .	10
3.2	AC Sweep . . . . .	10
3.3	Input Resistance Sweep . . . . .	11
3.4	Output Resistance Sweep . . . . .	11
3.5	Transient Sweep . . . . .	12
<b>4</b>	<b>Conclusion</b>	<b>12</b>
<b>5</b>	<b>References</b>	<b>12</b>

## List of Figures

1	Standard Common-Emitter Amplifier . . . . .	4
2	DC Equivalent Circuit . . . . .	5
3	Small-Signal Equivalent Circuit . . . . .	7
4	Small-Signal Equivalent with Values . . . . .	8
5	Final Common-Emitter Amplifier . . . . .	9
6	Bias Point Performance . . . . .	10
7	AC Sweep Gain Plot, Gain ( $A_{v_s}$ ) at 130 . . . . .	10
8	AC Sweep Input Impedance Plot, Approximately $Z_i = .44[\text{k}\Omega]$ . . .	11
9	AC Sweep Output Impedance Plot, Approximately $Z_o = .53[\text{k}\Omega]$ . .	11
10	Transient Sweep, Peak-to-Peak Output: $V_o = 6.2[\text{V}]$ . . . . .	12

## 1 Introduction

Common-emitter amplifiers are some of the most ubiquitous components of radio-frequency (RF) circuitry. These components, which rely on bipolar junction transistors (BJTs) involve the amplification of a source signal, passed through the base of the BJT. The base is connected to the collector branch via a resistor. To improve stability of such circuits, capacitors are added after the input and before the output, which allows for better direct-current (DC) filtration. Such amplification is crucial in audio-based circuits, like speakers, and radios, specifically antennas.

## 2 Circuit Design

We may begin with our provided model:

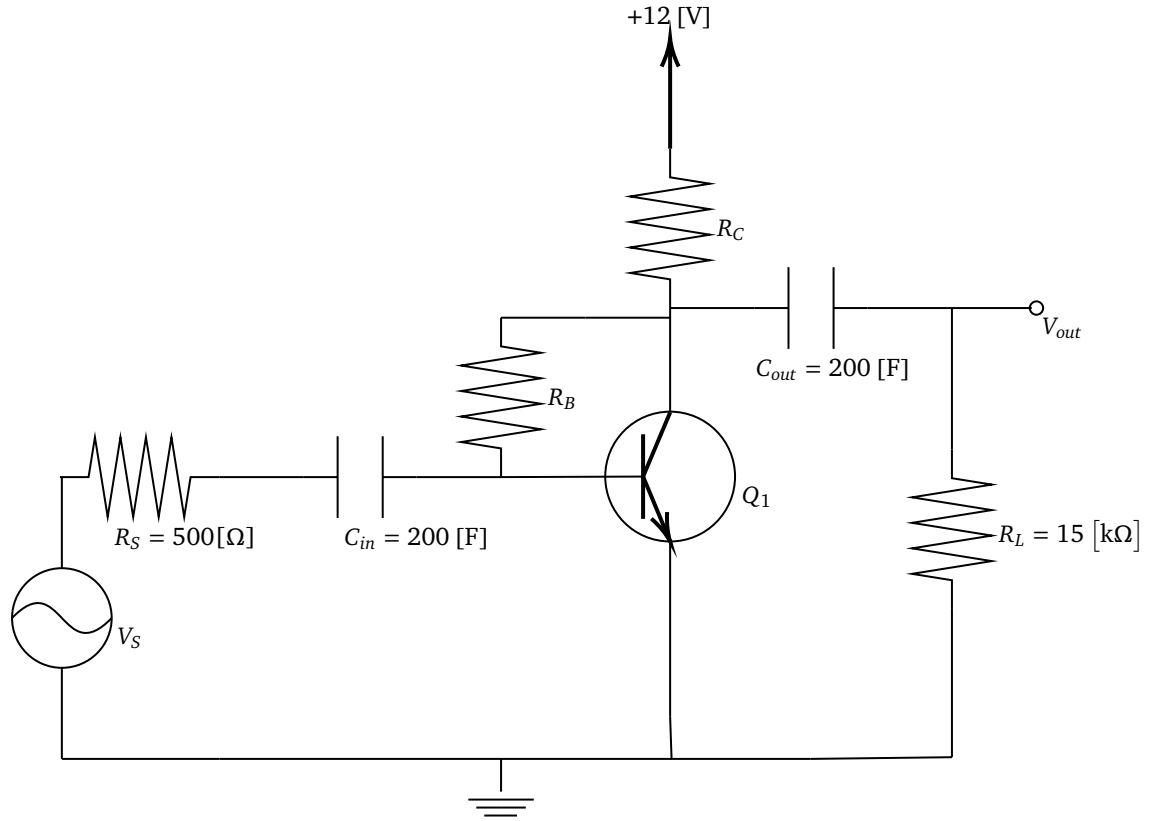


Figure 1: Standard Common-Emitter Amplifier

This, in tandem with the provided circuit example, will be the basis for our design.

## 2.1 Given Parameters

We are given the following parameters as a requirement for our amplifier:

$$\left\{ \begin{array}{ll} \text{Assume:} & T = 300[\text{K}] \\ |A_{VS}| = \frac{V_o}{V_{in}} & \geq 80 \\ I_C & \leq 8[\text{mA}] \\ V_{CC} & = 12[\text{V}] \\ R_S & = 500[\Omega] \\ R_L & = 15[\text{k}\Omega] \\ R_i & \approx R_S \\ V_{FB} & = .7[\text{V}] \\ \beta & = 200 \end{array} \right.$$

Finally, we want to ensure that there is a 7[V] peak-to-peak output signal swing without distortion. We begin by performing a DC analysis of the given circuit.

## 2.2 DC Analysis

The DC equivalent circuit may be constructed by taking all capacitors as open circuits. This gives us an equivalent circuit of:

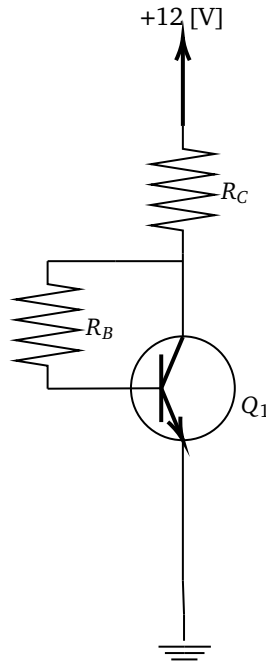


Figure 2: DC Equivalent Circuit

From this, we may use Kirchoff's voltage laws to write:

$$12 - (I_B + I_C)R_C - R_B I_B - V_{BE} = 0$$

We know  $\beta$ , which allows us to say:

$$200 = \frac{I_C}{I_B}$$

$$I_C = 200I_B$$

Substituting this into the above, we get:

$$12 - I_B(201R_C + R_B) - .7 = 0$$

### 2.2.1 Worst-Case Assumption

Since  $I_C \leq 8[\text{mA}]$ , we know that:

$$I_B \leq \frac{I_C}{200}$$

$$I_B \leq 40[\mu\text{A}]$$

### 2.2.2 Finding Applicable $R_B$ and $R_C$ Values

Assuming worst-case (*i.e.* highest) values of the currents, we get  $I_C = 8[\text{mA}]$  and  $I_B = 40[\mu\text{A}]$ . Plugging this in, we get:

$$11.3 = (40 \cdot 10^{-6})(201R_C + R_B)$$

$$282500 = 201R_C + R_B$$

$$R_C = \frac{282500 - R_B}{201}$$

We need  $R_B$  to be positive, which means  $201R_C < 282500$ . Let us take  $R_C$  as an arbitrary  $R_C = .9[\text{k}\Omega]$ , which gives us:

$$R_B = 101.6[\text{k}\Omega]$$

## 2.3 Small-Signal Analysis

We may redraw the circuit using the Hybrid- $\pi$  Model to obtain the small-signal equivalent:

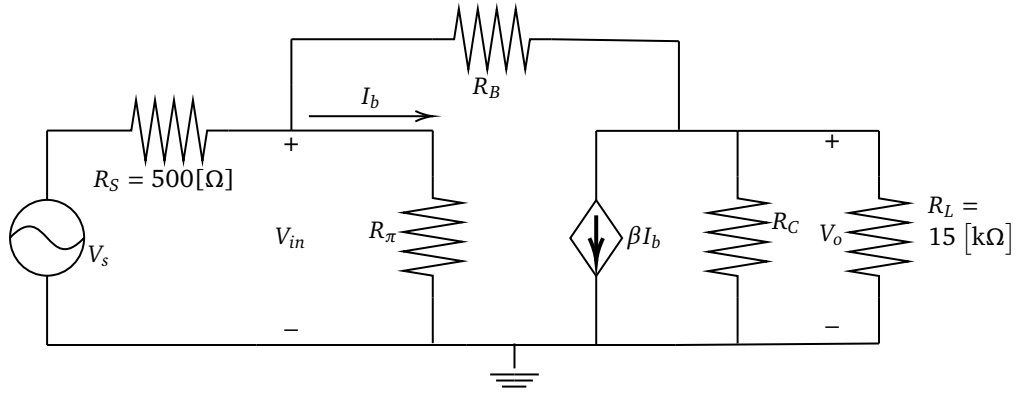


Figure 3: Small-Signal Equivalent Circuit

First and foremost, we must note that  $R'_L$  may be expressed as  $R_C || R_L$ . We can begin by finding:

$$g_m = \frac{I_C^{max}}{2V_T}$$

We take our quiescent collector current from the DC analysis to get:

$$g_m = \frac{8}{2(26)}$$

$$g_m = .1538$$

We then calculate  $R_\pi$  to get:

$$R_\pi = \frac{\beta}{g_m}$$

$$R_\pi = \frac{200}{.1538}$$

$$R_\pi = 1.3[\text{k}\Omega]$$

### 2.3.1 Input Impedance Calculation

Let us stop to verify that the input impedance is roughly equal to  $R_S$ . From our equivalent circuit, we may obtain:

$$R_i = \frac{(R_B + R'_L)R_\pi}{R_\pi + R_B + (\beta + 1)R'_L}$$

Let us get  $R'_L$  first:

$$R'_L = \frac{R_C R_L}{R_C + R_L}$$

$$R'_L = 849.06[\Omega]$$

We return to find the input impedance:

$$R_i = \frac{(101600 + 849.06)(1.3k)}{1.3k + 101600 + 849.06(201)}$$

$$R_i = 486.85[\Omega]$$

We see that, as intended, this is within 3% of the given value of  $R_S$ , and, thus, we may say that  $R_i \approx R_S$ .

### 2.3.2 Gain Calculation

From our equivalent circuit, we may conclude that the gain is:

$$|A_v| = \frac{R'_L(R_\pi - \beta R_B)}{R_\pi(R'_L + R_B)}$$

We substitute our values to get:

$$A_v = \frac{849.06(1300 - (200)(101600))}{1300(849.06 + 101600)}$$

$$A_v = -129.53$$

This meets the minimal gain requirement of  $|A_v| \geq 80$ . As such, our equivalent circuit becomes:

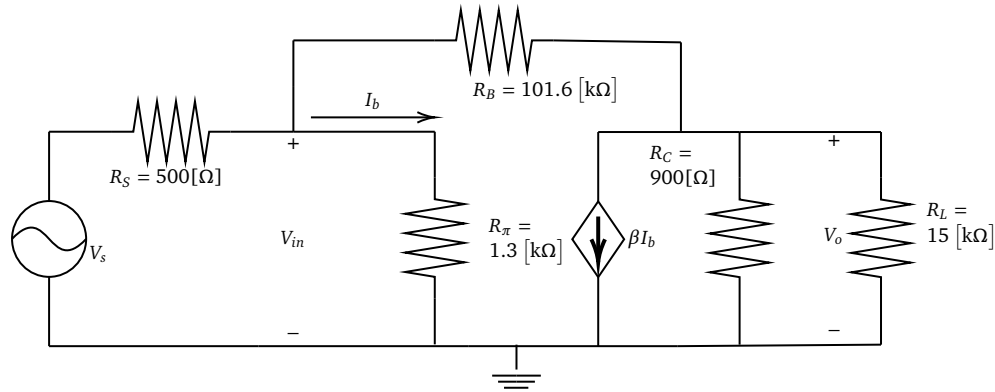


Figure 4: Small-Signal Equivalent with Values

This gives us our final circuit as:



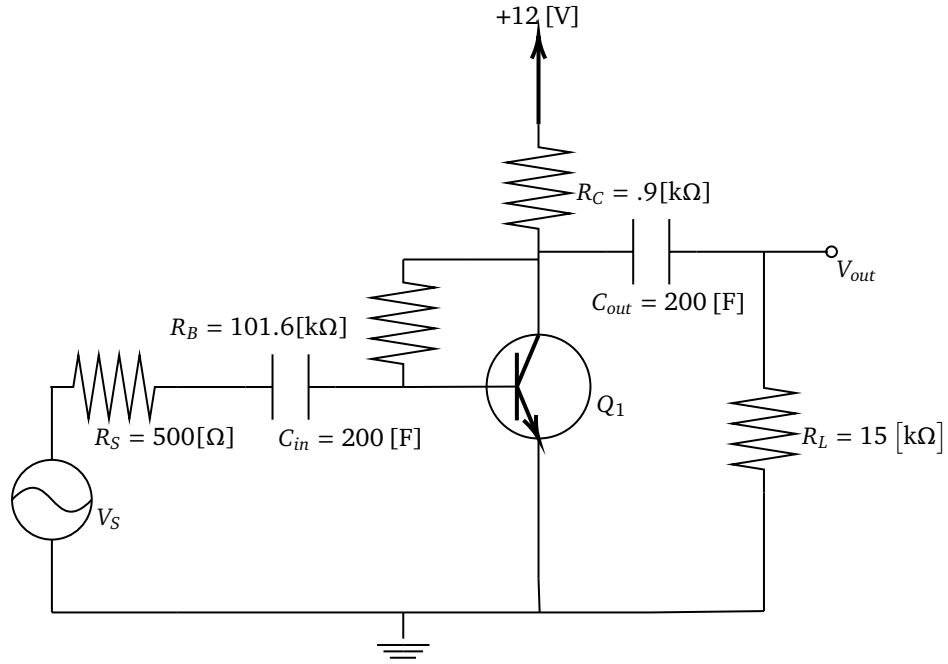


Figure 5: Final Common-Emitter Amplifier

### 2.3.3 Output Impedance Calculation

The final step is to calculate the expected output resistance. Based on the equivalent circuit in Figure 4, we get:

$$R_o = R_C || \left( \frac{R_B R_S + R_B R_\pi + R_S R_\pi}{(\beta + 1) R_S + R_\pi} \right)$$

We plug in known values to get:

$$\left( \frac{R_B R_S + R_B R_\pi + R_S R_\pi}{(\beta + 1) R_S + R_\pi} \right) = \frac{(101600)(500) + (101600)(1300) + (500)(1300)}{(201)(500) + 1300}$$

$$\left( \frac{R_B R_S + R_B R_\pi + R_S R_\pi}{(\beta + 1) R_S + R_\pi} \right) = 1802.8 [\Omega]$$

Then, we calculate  $R_C || 1802.8$ :

$$R_o = \frac{(1802.8)(900)}{900 + 1802.8}$$

$R_o = 600.32 [\Omega]$

### 3 Simulation

#### 3.1 Bias Point Performance

Simulating in PSPICE, we obtain the following Bias Point Performance:

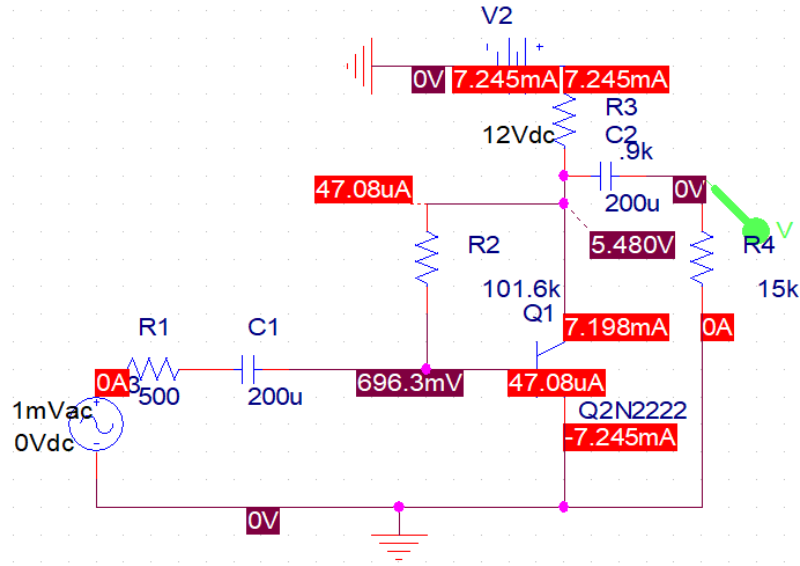


Figure 6: Bias Point Performance

We may observe, that, as calculated, the collector current,  $I_C = 7.198[\text{mA}] \leq 8[\text{mA}]$ .

#### 3.2 AC Sweep

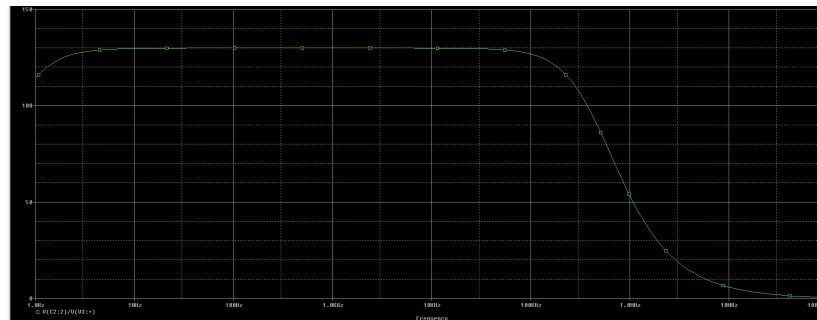


Figure 7: AC Sweep Gain Plot, Gain ( $A_{vS}$ ) at 130

We may observe that the gain is right at the expected value, or approximately at a magnitude of 130 at midband values.

### 3.3 Input Resistance Sweep

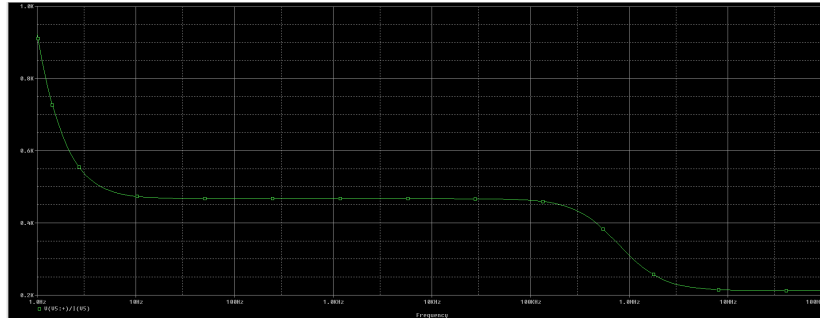


Figure 8: AC Sweep Input Impedance Plot, Approximately  $Z_i = .44[\text{k}\Omega]$

The resulting input impedance is very close to the calculated one. We may observe that the calculated impedance was  $.486[\text{k}\Omega]$ , while the simulated one is a bit less. These values are still quite similar, and, as such, close enough to the expected one at midband values.

### 3.4 Output Resistance Sweep

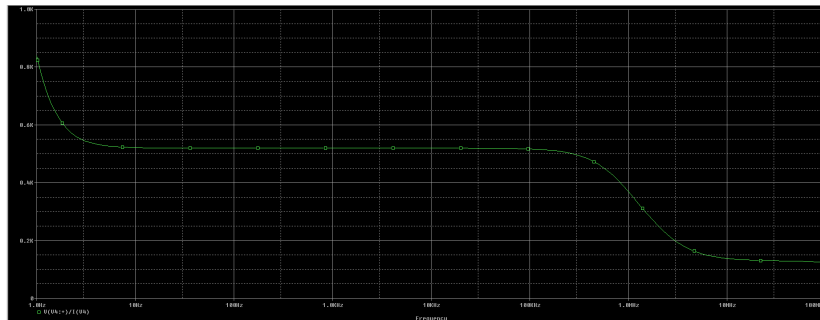


Figure 9: AC Sweep Output Impedance Plot, Approximately  $Z_o = .53[\text{k}\Omega]$

Once again, we see that the simulated value is a bit less than the calculated value. The calculated output impedance is  $.6[\text{k}\Omega]$ , while the one observed above is  $.53[\text{k}\Omega]$  at midband values.

### 3.5 Transient Sweep

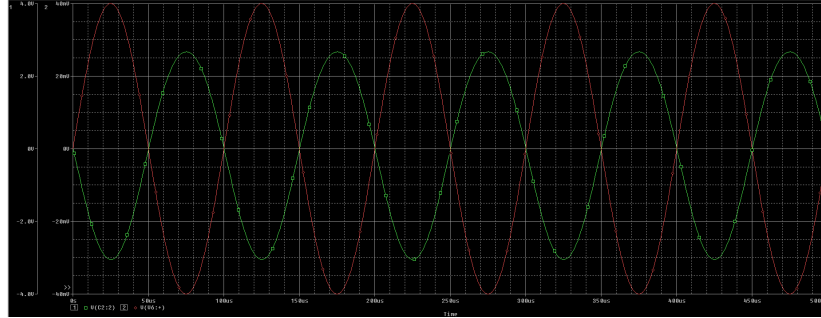


Figure 10: Transient Sweep, Peak-to-Peak Output:  $V_o = 6.2[V]$

We may calculate the voltage gain as:

$$A_{vs} = \frac{6.2}{.04} = 155$$

We see that the transient simulation has a slightly higher gain than the AC sweep and the calculated one. Again, the values are close enough that nothing is too out of the ordinary.

## 4 Conclusion

We may observe the following obtained values:

Value	Specified	Calculated	Simulated	Requirement Met?
Gain ( $A_{vs}$ )	$\geq 80$	129.53	130/155	✓
Input $Z_i$	$\approx 500[\Omega]$	486.85 $[\Omega]$	440 $[\Omega]$	✓
Collector Current ( $I_C$ )	$\leq 8[mA]$	$\leq 8[mA]$	7.198 $[mA]$	✓

As such, we see that we were able to successfully meet and even exceed the given requirements.

## 5 References

Allan R. Hambley, *Electronics, 2nd edition, Prentice Hall, 1999* 1999