

Lab Three  
Fundamentals of Electronics  
EECE2412/3

Michael BRODSKIY  
Brodskiy.M@Northeastern.edu

October 29, 2024

Date Performed:	October 15/22, 2024
Partner:	Rahul SINGH
Instructor:	Professor ONABAJO
TAs:	Ming XIANG & Amr KASSAB

### **Abstract**

The goal of this laboratory experiment is to orient the performing individual with bipolar junction transistors (BJTs). Common regions (active, saturated, and cut-off) are explored, in addition to the effects of temperature variance on BJT performance. Finally, a light-emitting diode (LED) light-sensing circuit is constructed with a photocell.

KEYWORDS: BJT, active, saturated, cut-off, temperature variance, LED, photocell

## Contents

<b>1</b>	<b>Equipment</b>	<b>4</b>
<b>2</b>	<b>Experimental Procedure</b>	<b>5</b>
2.1	The Forward-Active Region (with varying $\beta$ ) . . . . .	5
2.1.1	Using Curve Tracers . . . . .	6
2.1.2	Tolerance and Standard Deviation of Gain . . . . .	6
2.1.3	Thermal Response . . . . .	7
2.2	BJT Saturation . . . . .	7
2.3	BJT Cut-Off . . . . .	8
<b>3</b>	<b>Conclusion</b>	<b>8</b>

## List of Figures

1	BJT Biasing Circuit . . . . .	5
---	-------------------------------	---

# 1 Equipment

Available equipment included:

- 2N3904 Bipolar Junction Transistors
- Light-Emitting Diodes (varying colors)
- Basic Circuit Components (Wires, Inductors, Capacitors, etc.)
- Keysight EDU36311A Dual DC Power Supply
- Photocell (Light-Varying Resistor)

## 2 Experimental Procedure

We begin by constructing the following circuit:

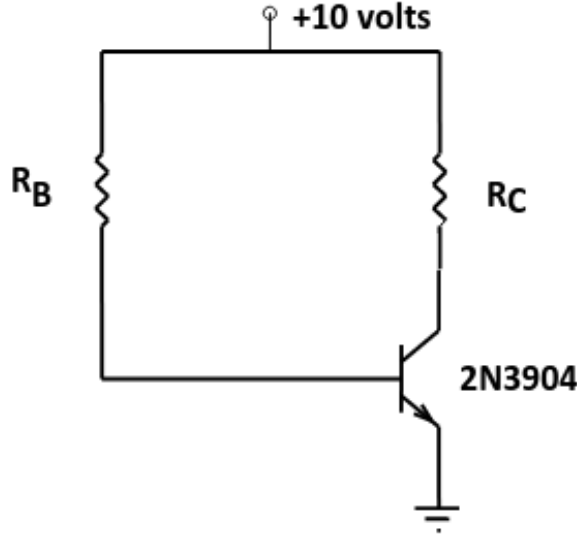


Figure 1: BJT Biasing Circuit

We proceed to test various configurations which place the 2N3904 in common regions, such as active, saturated, and cut-off.

### 2.1 The Forward-Active Region (with varying $\beta$ )

Using the circuit shown in Figure 1, with  $R_B = 316.7[\text{k}\Omega]$  and  $R_C = 1.003[\text{k}\Omega]$ , we place the BJT into its active region (supporting calculations are present in the pre-lab). Measuring  $V_{CE}$  and  $V_{BE}$  for both of our BJTs, we find:

$$V_{BE_1} = .708[\text{V}] \quad \text{and} \quad V_{CE_1} = 3.394[\text{V}]$$

$$V_{BE_2} = .704[\text{V}] \quad \text{and} \quad V_{CE_2} = 3.378[\text{V}]$$

We know the BJT is in its active region since, based on the above measurements,  $V_{CE} > V_{BE}$  (or, alternatively  $V_{BE} > 0$  and  $V_{BC} < 0$ ).

Using the data from above, we may calculate  $I_B$ ,  $I_C$ , and  $\beta$ :

$$I_{B_1} = \frac{10 - .708}{316.7k} \quad \text{and} \quad I_{C_1} = \frac{10 - 3.394}{1003}$$

$$I_{B_1} = 29.34[\mu\text{A}] \quad \text{and} \quad I_{C_1} = 6.586[\text{mA}]$$

$$I_{B_2} = \frac{10 - .704}{316.7k} \quad \text{and} \quad I_{C_1} = \frac{10 - 3.378}{1003}$$

$$I_{B_1} = 29.353[\mu A] \quad \text{and} \quad I_{C_1} = 6.6022[mA]$$

From this, we find the direct current (DC) gains:

$$\beta_1 = \frac{6.586}{.02934}$$

$$\beta_1 = 224.47$$

$$\beta_2 = \frac{6.6022}{.029353}$$

$$\beta_2 = 224.92$$

### 2.1.1 Using Curve Tracers

Per the curve tracer presented in class, we would expect  $I_B = 40[\mu A]$  for our  $I_C$  value. This gives us a  $\beta$  of:

$$\beta_{curve} = \frac{6}{.04}$$

$$\beta_{curve} = 150$$

### 2.1.2 Tolerance and Standard Deviation of Gain

It would be difficult to design a circuit with  $\beta = 150 \pm 1\%$  because, even within the same model of BJT, there is much variation; however, it should still be practical to meet this strict tolerance. This is further supported by the variance of  $\beta$  presented in the BJT data sheets attached to the laboratory experiment. Though the tested transistors are all within specification, there is a great amount of variance, which we can calculate using the standard deviation. We obtain two of each  $\beta$  value from other groups:

$$\beta_1 = 186, 196$$

$$\beta_2 = 201, 217$$

The average of the gains is:

$$\beta_1^{avg} = 202.16$$

$$\beta_2^{avg} = 214.31$$

Thus, we get standard deviations of:

$$\sigma_{\beta_1} = 19.96 \quad \text{and} \quad \sigma_{\beta_2} = 12.185$$

We may see that these standard deviations are all, more or less, within 1% (for  $\beta_1$  it is above for two of the three values), and, therefore, we should be able to design for such a tolerance.

### 2.1.3 Thermal Response

Using a can of refrigerant, we obtain new values:

$$V_{CE} = 3.78[\text{V}] \quad \text{and} \quad V_{BE} = .725[\text{V}]$$

This gives us:

$$\beta = \frac{\left(\frac{10 - 3.78}{1003}\right)}{\left(\frac{10 - .725}{316700}\right)}$$

$$\boxed{\beta_{cold} = 211.48}$$

Per the data sheets, we would expect a drop in  $I_C$ , which would result in a decrease in  $\beta$ , as shown above. This would be unwanted in a car stereo system, as colder weather would mean that the amplification would not be as great, thus causing lower volumes.

## 2.2 BJT Saturation

As per the pre-lab, we know that  $R_B \leq 208.66[\text{k}\Omega]$  will saturate the BJT. Thus, we select the closest available value:  $R_B = 157[\text{k}\Omega]$ . Measuring the saturation values, we find:

$$V_{CE_1}^{sat} = 45[\text{mV}] \quad \text{and} \quad V_{BE_1}^{sat} = .906[\text{V}]$$

$$V_{CE_2}^{sat} = 51.5[\text{mV}] \quad \text{and} \quad V_{BE_1}^{sat} = .94[\text{V}]$$

We see that there is a lot of variation between even the same model of BJT, and, thus, it is necessary to account for BJT-to-BJT variation. We may find the  $\beta$  values for this region:

$$I_{B_1} = \frac{10 - .906}{157000} \quad \text{and} \quad I_{C_1} = \frac{10 - .045}{1003}$$

$$\boxed{I_{B_1} = 57.92[\mu\text{A}] \quad \text{and} \quad I_{C_1} = 9.925[\text{mA}]}$$

$$I_{B_2} = \frac{10 - .94}{157000} \quad \text{and} \quad I_{C_2} = \frac{10 - .0515}{1003}$$

$$\boxed{I_{B_1} = 57.7[\mu\text{A}] \quad \text{and} \quad I_{C_1} = 9.9187[\text{mA}]}$$

This gives us:

$$\beta_1 = \frac{9.925}{.05792}$$

$$\boxed{\beta_1 = 171.36}$$

$$\beta_2 = \frac{9.9187}{.0577}$$

$$\boxed{\beta_2 = 171.90}$$

From this, we see that, if a high  $\beta$  is important in a circuit, we want to operate in the active, and not in the saturated region.

### 2.3 BJT Cut-Off

Using the different methods provided, we obtain:

$$V_{CE_1} = 10[\text{V}]$$

$$V_{CE_2} = 9.638[\text{V}]$$

$$V_{CE_3} = 4.572[\text{V}] \quad (\text{when } R = 470[\Omega])$$

### 2.4 BJT Touch-Sensitive Switch

## 3 Conclusion