

Homework 7

Michael Brodskiy

Professor: M. Onabajo

November 1, 2024

1. We may begin by finding the DC equivalent by changing all capacitors to open circuits.
This gets us:

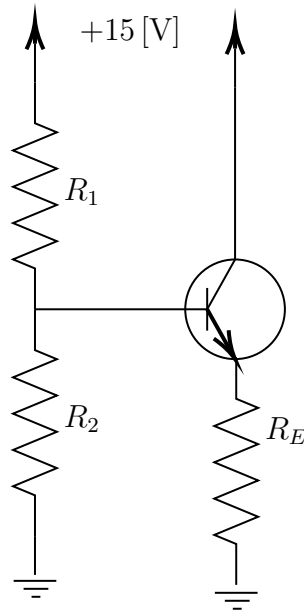


Figure 1: DC Equivalent Circuit

We can find a Thévenin equivalent for the R_1 - R_2 voltage as:

$$V_{th} = 15 \left[\frac{10k}{10k + 10k} \right]$$
$$V_{th} = 7.5\text{[V]}$$

And then the equivalent resistance:

$$R_{th} = \frac{10^2}{20}$$

$$R_{th} = 5[\text{k}\Omega]$$

This allows us to draw the circuit as:

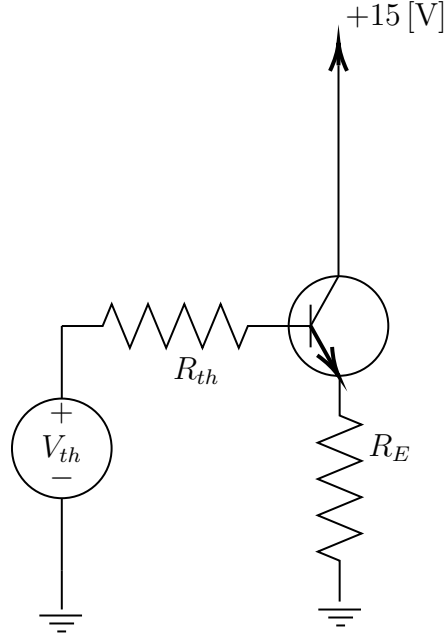


Figure 2: DC Equivalent Simplified

We use KVL at the base-emitter loop to get

$$-V_{th} + I_B R_{th} + V_{BE} + I_E R_E = 0$$

Since we know $I_E = (1 + \beta)I_B$, we may write:

$$-V_{th} + I_B R_{th} + V_{BE} + (1 + \beta)I_B R_E = 0$$

Rearranging, we get:

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta)R_E}$$

We plug in our known values to get:

$$I_B = \frac{7.5 - .7}{5k + (1 + 100)1k}$$

$$I_B = 64.151[\mu\text{A}]$$

From this, we may find:

$$\begin{aligned} I_{CQ} &= \beta I_B \\ I_{CQ} &= (100)(64.151 \cdot 10^{-6}) \\ I_{CQ} &= 6.4151[\text{mA}] \end{aligned}$$

We can find r_π by using the equation:

$$r_\pi = \frac{\beta}{g_m}$$

Where $g_m = \frac{I_{CQ}}{V_T}$:

$$\begin{aligned} r_\pi &= \frac{\beta V_T}{I_{CQ}} \\ r_\pi &= \frac{100(.026)}{.0064151} \\ r_\pi &= 405.29[\Omega] \end{aligned}$$

We can then perform a small-signal analysis by finding r_e :

$$\begin{aligned} r_e &= \frac{\beta V_T}{(1 + \beta)I_{CQ}} \\ r_e &= 4.0128[\Omega] \end{aligned}$$

Using this, we can use our small-signal analysis model to find the gain. First, we get:

$$V_o = V_i \left[\frac{R_E R_L}{(R_E + R_L)r_e + R_E R_L} \right]$$

Thus, we see that the voltage gain is:

$$A_v = \left[\frac{R_E R_L}{(R_E + R_L)r_e + R_E R_L} \right]$$

We plug in our known values to find:

$$\begin{aligned} A_v &= \left[\frac{(1000)(500)}{(1500)(4.0128) + (500000)} \right] \\ A_v &= .9881 \end{aligned}$$

Furthermore, we can find the open-loop voltage gain when $R_L \rightarrow \infty$:

$$A_{voc} = \left[\frac{R_E}{r_e + R_E} \right]$$

$$A_{voc} = \left[\frac{1000}{4.0128 + 1000} \right]$$

$$\boxed{A_{voc} = .996}$$

Now, we can work to find the input impedance. First and foremost, we know:

$$i_e = V_i \left[\frac{R_E R_L}{(R_E + R_L)r_e + R_E R_L} \right]$$

Using KCL for the input current node, we may observe:

$$i_i + \frac{\beta}{\beta + 1} i_e = V_i \left[\frac{R_1 + R_2}{R_1 R_2} \right] + i_e$$

We can rearrange this to find:

$$\frac{V_i}{i_i} = \left[\frac{R_1 + R_2}{R_1 R_2} + \frac{R_E + R_L}{(1 + \beta)[(R_E + R_L)r_e + R_E R_L]} \right]^{-1}$$

$$Z_i = (2.2935 \cdot 10^{-4})^{-1}$$

$$\boxed{Z_i = 4360.2[\Omega]}$$

The current gain may be expressed as the ratio of input (Z_i) and output (R_L) impedances:

$$A_i = A_v \frac{Z_i}{R_L}$$

$$\boxed{A_i = 8.6854}$$

From here, we know the power gain is:

$$G = A_i A_v$$

$$G = (.996)(8.6854)$$

$$\boxed{G = 8.6507}$$

Finally, we can find the output resistant by computing several parallel resistances:

$$Z_o = R_E \parallel \left[\frac{R_B \parallel R_S + r_\pi}{\beta + 1} \right]$$

We plug in known values:

$$Z_o = 1k \parallel \left[\frac{833 + 405.29}{101} \right]$$

$$Z_o = 1k \parallel 12.264$$

$$\boxed{Z_o = 12.115[\Omega]}$$

2. We begin by investigating $V_{hum} \rightarrow 0$, which shows that the circuit is the same for both figures:

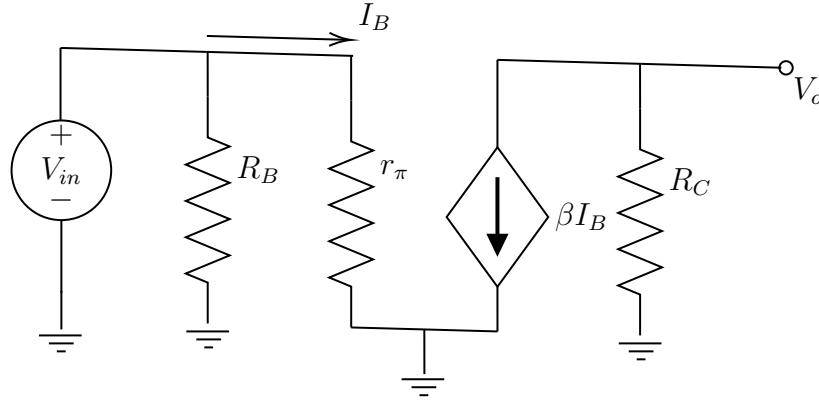


Figure 3: Equivalent Circuit is the Same for $V_{hum} \rightarrow 0$

From this, we may observe that:

$$\boxed{A_v \approx -\frac{\beta R_C}{r_\pi}}$$

We can then investigate the case when $V_{hum} \neq 0$ and $V_{in} \rightarrow 0$. For the first figure, we see:

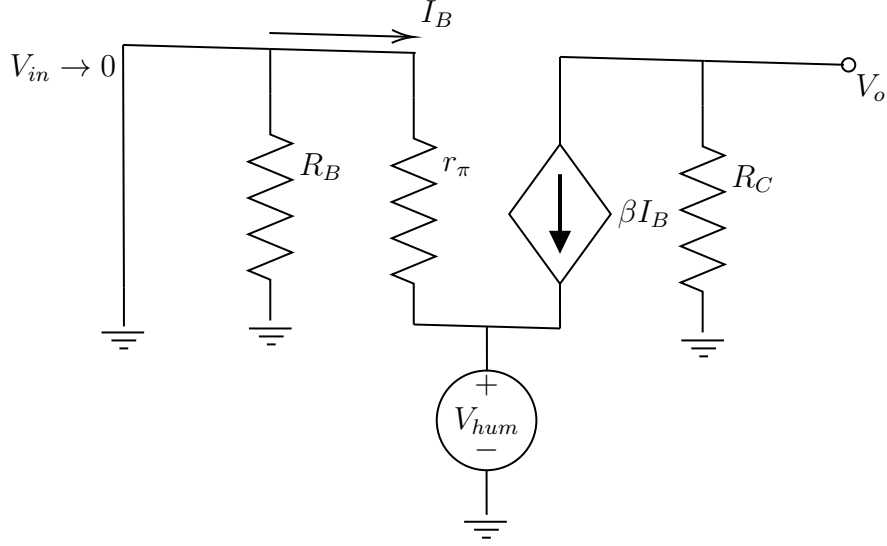


Figure 4: Equivalent Circuit for Figure (a) as $V_{in} \rightarrow 0$

We may conclude that the hum gain can be expressed as:

$$A_{(a)} = \frac{\beta R_C}{r_\pi}$$

Finally, we may draw the equivalent circuit for the second figure to get:

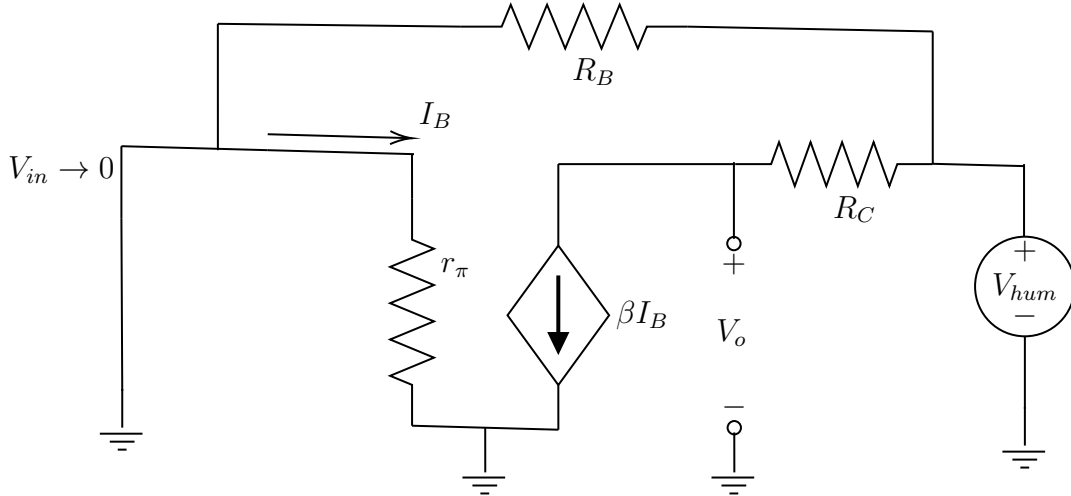


Figure 5: Equivalent Circuit for Figure (b) as $V_{in} \rightarrow 0$

First, note that $V_o = V_{hum}$ since the base current, $I_B = 0$, which causes the current-controlled current source to become null as well. As such, we may write that, for the second circuit, there is no gain, as the output is equivalent to the input, and thus:

$$\boxed{A_{(b)} = 1}$$

We can calculate the gain for the provided values by first finding r_π :

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

We can perform analyses through the loops to write:

$$I_{BQ} = \frac{V_{CC} - .7}{R_B} \quad \text{and} \quad I_{CQ} = \beta I_{BQ}$$

This gives us:

$$\begin{aligned} I_{BQ} &= \frac{15 - .7}{1M} \\ I_{BQ} &= 14.3[\mu A] \end{aligned}$$

Consequently, we find:

$$I_{CQ} = 1.43[\text{mA}]$$

This gives us:

$$\begin{aligned} r_\pi &= \frac{100(.026)}{1.43 \cdot 10^{-3}} \\ r_\pi &= 1.818[\text{k}\Omega] \end{aligned}$$

We can then find:

$$\begin{aligned} A_{(a)} &= \frac{(100)(4700)}{1818} \\ \boxed{A_{(a)} &= 258.8} \end{aligned}$$

We know that when $V_{hum} \rightarrow 0$, the gain becomes the negative of the above. As such, we find the following values:

$$\left\{ \begin{array}{ll} A_{v(a)} &= -258.8 \\ A_{hum(a)} &= 258.8 \\ A_{v(b)} &= -258.8 \\ A_{hum(b)} &= 1 \end{array} \right.$$

3.