

Voltage Gain: $A_v = \frac{v_o}{v_i}$

Current Gain: $A_i = \frac{i_o}{i_i}$

Power Gain: $G = A_v A_i$

Decibel: $A_{v\text{dB}} = 20 \log(|A_v|)$

$A_{i\text{dB}} = 20 \log(|A_i|)$

$G_{\text{dB}} = 10 \log(|G|)$

<p>Energy Conservation: $P_i + P_s = P_o + P_d \longrightarrow \begin{cases} P_i & = \text{Power from Source} \\ P_s & = \text{Power from DC Supplies} \\ P_o & = \text{Output Power at Load} \\ P_d & = \text{Power Dissipated in the Op-Amp} \end{cases}$</p>
--

Frequency Dependence:

Capacitor: $Z_c = \frac{1}{j\omega C}$

Inductor: $Z_L = j\omega L$

Summing Point Constraint:

- Only applies when the op-amp is in negative feedback
- Assuming ideal op-amp, $V_+ - V_- = 0$ (no current at terminals)
- For non-ideal op-amps: $V_o = A(s)(V_+ - V_-)$

$f_{3\text{dB}} = \frac{\omega_{3\text{dB}}}{2\pi}$

$\text{GBW} = |A_v| f_{3\text{dB}}$

Diodes:

- In Forward Bias (FB): Permit current flow, have a positive voltage drop
- In Reverse Bias (RB): No current flow (open circuit)
 - Constant Voltage Drop (CVD): Diodes have same forward-bias drop ($\approx .7\text{V}$)
- Assume bias mode for each diode in diagram, calculate values to verify assumptions
- CVD + resistance model: $r_d = \frac{nV_T}{I_{DQ}}$ (approximated around quiescent point, Q)

$I_D = I_s e^{\frac{V_D}{nV_T}} + 1$ Room Temp: $V_T \approx 26\text{mV}$ $1 < n < 2$ $10^{-6} < I_s < 10^{-18}\text{A}$

Temp Dependence: constant $I \rightarrow V$ drop decreases $\approx 2\text{mV}$ per 1°C temperature increase
--

Zener Diodes: $V_D = -V_{zo} - I_z r_z$ in breakdown, with $I_z = -I_D > 0$

Transformers: step voltages according to turns ratio ($N_p : N_s$) or ($n : 1$), with $V_s = V_p/n$

BJT Regions

EBJ	CBJ	Mode
FB	RB	Active
FB	FB	Saturation
RB	RB	Cutoff

Note: When designing an amplifier confirm that the BJT is in the active region

BJT Formulas

$$I_E = I_C + I_B$$

$$I_E = I_{ES} \left[e^{\frac{V_{BE}}{V_T}} - 1 \right]$$

Active Region Only:







$$I_C = \alpha I_E$$

$$I_B = (1 - \alpha) I_E$$

$$I_C = \beta I_B$$

$$I_S = \alpha I_{ES}$$

For BJTs:	$\beta = \frac{\alpha}{1 - \alpha}$	$\alpha = \frac{\beta}{1 + \beta}$	Typically: $\alpha \approx 1$, and $I_C \approx I_E$ but $I_C < I_E$
-----------	-------------------------------------	------------------------------------	---

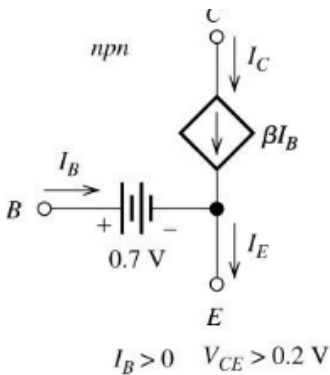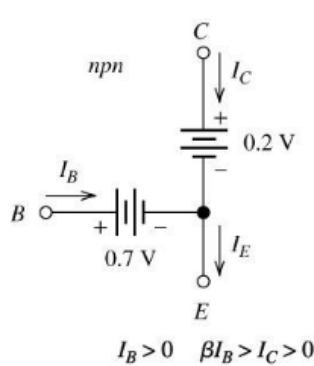 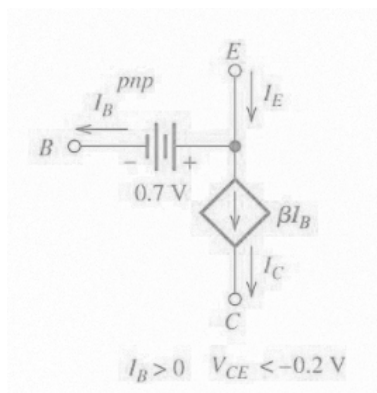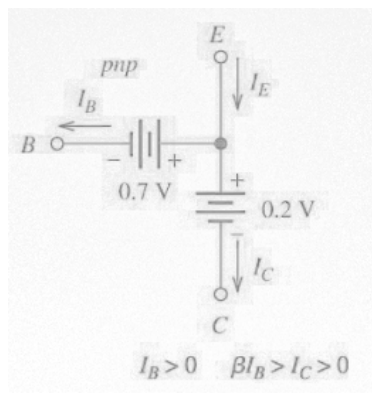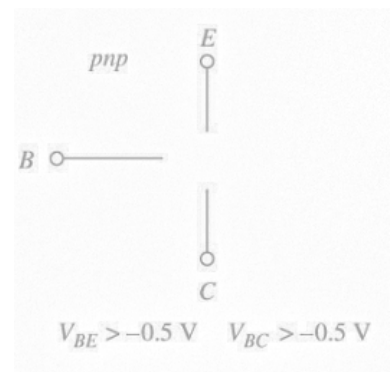BJT ModelsFigure 1: *npn* in Active ModeFigure 2: *npn* in SaturationFigure 3: *npn* in CutoffFigure 4: *pnp* in Active ModeFigure 5: *pnp* in SaturationFigure 6: *pnp* in Cutoff

Small-Signal Equivalent ($|V_{BE}| < 10[\text{mV}] \ll V_T$)

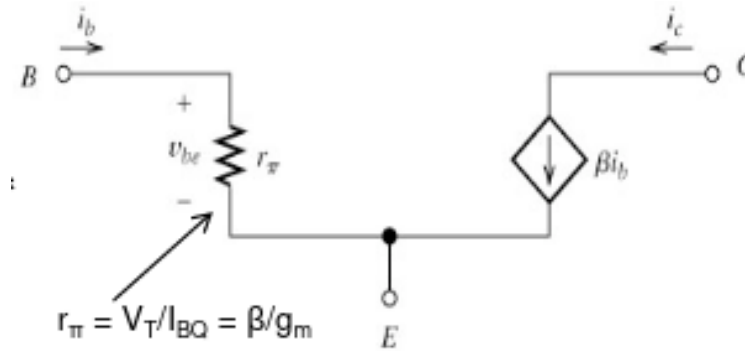
 
 
Figure 7: Small Signal Equivalent for *nnp/pnp*'sFigure 8: Hybrid π Model

Figure 9: T-Model

Small-Signal Formulas

$$g_m = \frac{I_{CQ}}{V_T} = \frac{\alpha}{r_e}$$

$$r_\pi = \frac{V_T}{I_{BQ}} = \frac{\beta}{g_m}$$

$$r_{ce} = \frac{V_{early}}{I_{CQ}}$$

$$r_e = \frac{V_T}{I_{EQ}} = \frac{V_T}{(1 + \beta)I_{BQ}} = \frac{r_\pi}{1 + \beta}$$

When r_{ce} not specified or $r_{ce} \gg R_L$ and r_e , then it can be removed

• MOSFET Regions

1. Cutoff ($V_{GS} < V_{to}$)
2. Triode ($V_{GS} > V_{to}, V_{DS} < V_{GS} - V_{to}$)
3. Saturation ($V_{GS} > V_{to}, V_{DS} > V_{GS} - V_{to}$)

- Triode — $\left(\frac{W}{L}\right) \left(\frac{KP}{2}\right) [2(V_{GS} - V_{to})V_{DS} - V_{DS}^2](1 + \lambda V_{DS})$
- Saturation — $\left(\frac{W}{L}\right) \left(\frac{KP}{2}\right) (V_{GS} - V_{to})^2(1 + \lambda V_{DS})$
- TS Boundary — $\left(\frac{W}{L}\right) \left(\frac{KP}{2}\right) V_{DS}^2$

• Drain Currents

- Cutoff — $I_D = 0$

- For PMOS case, $V_{SG} = -V_{GS}$ and $V_{SD} = -V_{DS}$, $V_{to} < 0 \rightarrow |V_{to}|$ in formulas, and reversed reference direction

MOSFET Small Signal Model

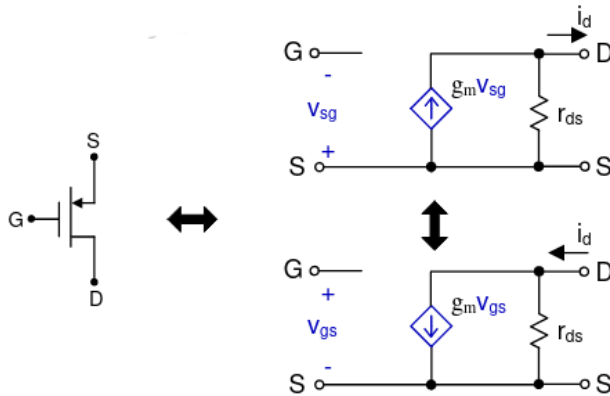


Figure 10: P (top) and N (bot) in Sat

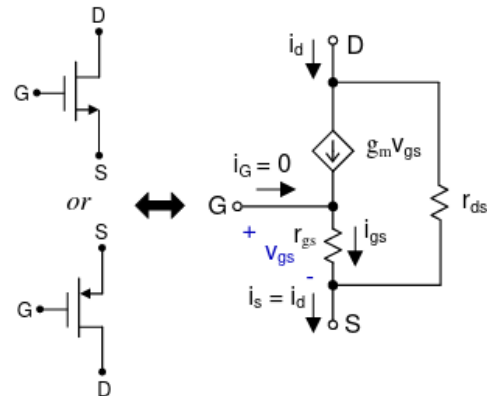


Figure 11: T-Model for MOSFETs

MOSFET Saturation Formulas:

$$r_{gs} = \frac{1}{g_m}$$

$$r_{ds} = \frac{1}{\lambda I_D} = \frac{|V_A|}{I_D}$$

$$g_m = \frac{2I_D}{V_{GSQ} - V_{to}} = KP \frac{W}{L} (V_{GSQ} - V_{to}) = \sqrt{2KP \frac{W}{L} I_D}$$

MOSFET Triode Formulas:

Simply becomes a resistor with value r_{on} .

$$r_{on} = \left[KP \frac{W}{L} (V_{GSQ} - V_{to}) \right]^{-1}$$

De Morgan's Laws:

$$\overline{A + B} = \bar{A} \bar{B}$$

$$\overline{AB} = \bar{A} + \bar{B}$$

CMOS Network Building:

PUN: Negate Individual Inputs

PDN: Negate Overall Input

Inputs in series are “AND”-ed and inputs in parallel are “OR”-ed