

# Lecture 5

Michael Brodskiy

Professor: M. Onabajo

September 19, 2024

- Finite Open-Loop Gain and Bandwidth
  - Assumptions during most previous examples
    - \* Infinite  $A_{0OL}$  (subscript “0” indicates DC gain)
    - \* Gain independence with respect to frequency (“flat gain”)
  - Open-loop gain of a typical (real) op-amp:
    - \* Single-pole approximation ( $F_{BOL}$  = break frequency)
    - \* High-frequency roll-off with  $-20\text{dB/dec}$  (single-pole approximation — for first order filters, can approximate  $f_t = A_{0OL}f_{BOL}$ )
    - \*  $f_t$  = transition frequency (unity-gain)
- Mathematical Representation of Finite Gain/Bandwidth
  - $A_{0OL}$  = DC gain,  $\omega_B$  = break frequency,  $\omega_t$  = unity-gain frequency
  - Op-amp model with a transfer function of a single-pole low-pass filter:

$$A(\omega) = \frac{A_{0OL}}{1 + (j\omega/\omega_B)}, \quad |A(\omega)| = \frac{A_{0OL}}{\sqrt{1 + \left(\frac{\omega}{\omega_B}\right)^2}}$$

- Inverting Amplifier Analysis
  - High closed-loop gain (high  $R_2/R_1$  ratio) reduces the closed-loop break frequency
- Closed-Loop Gain versus Break Frequency Trade-off
  - Fundamental gain-bandwidth (GBW) product limitation:

$$f_t = A_{0OL}f_{BOL} = A_{0CL}f_{BCL}$$

- When  $f \gg f_B$ :

$$|A(f)| \approx A_{0OL} \cdot \frac{f_B}{f} = \frac{f_t}{f}$$

- Closed-Loop: Gain Bandwidth  $\propto f_{3dB}$

- When an op-amp is connected in a feedback configuration, the gain-bandwidth product ( $f_t$ ) remains unchanged
- The 3dB frequency (break frequency) depends on feedback network components
- Gain-bandwidth product ( $f_t = A_{0OL}f_{BOL}$ )

- Large-Signal Operation: Voltage Swing

- Output voltage swing limitation
  - \* The output voltage can only be in the following range:

$$V_{S-} + x < V_o < V_{S+} - x$$

- \* The output limits should be specified in the manufacturers datasheet
- Clipping (saturation) occurs if the above condition is not met

- Linear Operating Range

- The input/output transfer characteristic of an op-amp (with a specified supply) voltage provide valuable information about large-signal operation

- Large-Signal Operation: Current Restrictions

- Op-amps have specified output current limits
- The op-amp must source/sink the current to/from load impedance (and feedback network elements)
- Careful: Small load or feedback resistors  $\rightarrow$  high  $I_o$
- Clipping occurs when  $I_o > I_{\text{limit}}$  would be required, but  $I_o = I_{\text{limit}}$

- Finite Open-Loop Gain and Bandwidth

$$A(f) = \frac{A_{0OL}}{1 + j(f/f_{BOL})}$$

- Closed-Loop Impact of Finite Gain/Bandwidth

- \* Inverting amplifier:  $G = -\frac{R_2}{R_1}$
- \* Non-inverting amplifier:  $G = 1 + \frac{R_2}{R_1}$
- \* For both cases:  $f_{3dB} \approx \frac{f_t}{1+(R_2/R_1)}$

- Output Slew-Rate Limitation

$$\left| \frac{dv_o(t)}{dt} \right| \leq SR$$

- The magnitude of the output voltage's rate of change can not exceed the slew-rate ( $SR$ ) specification of the op-amp
- Typical  $10^5[\text{V/s}] < SR < 10^8[\text{V/s}]$
- Usually the  $SR$  is specified with load resistance conditions

- DC Imperfections of Op-Amps

- Bias Current ( $I_B$ )
  - \* Required for proper operation of internal circuitry (or resulting from unwanted leakage currents)
  - \* Typical range:  $0.1[\text{nA}] - 1[\mu\text{A}]$
  - \*  $I_B = (I_{B+} - I_{B-})/2$
  - \*  $I_{B+}$  and  $I_{B-}$  flow at the respective terminals
- Offset Current ( $I_{off}$ )
  - \*  $|\pm I_{off}| = |I_{B+} - I_{B-}| < 200[\text{nA}]$  normally
  - \* Results from internal device mismatches (transistors, resistors, etc.)
- Offset Voltage ( $V_{off}$ )
  - \* Due to internal device mismatches
  - \*  $|\pm V_{off}| < \text{a few millivolts}$

- Analysis Procedure with DC Imperfections

- Draw a schematic diagram in which the source for a single DC imperfection is included (modeled)
- Replace all other sources
  - \* Voltage source  $\rightarrow$  short circuit
  - \* Current source  $\rightarrow$  open circuit
- Follow standard circuit analysis laws and ideal op-amp assumptions