Lecture 17

Michael Brodskiy

Professor: M. Onabajo

December 2, 2024

 \bullet When designing logic circuits, we want to choose transistor widths such that $t_{PLH} \approx t_{PHL}$