

Lecture 3

Michael Brodskiy

Professor: M. Onabajo

September 9, 2024

- Frequency Dependence (Impedance)

- Capacitor

$$Z_c = \frac{1}{j\omega C}$$

- Inductors

$$Z_L = j\omega L = SL$$

- Note, for capacitors impedance decreases with frequency, while it increases with frequency for inductors

- DC Coupling

- Amplifier stages are directly connected together
- High-frequency gain decreases (“rolls off”) due to unwanted (“parasitic”) capacitances and inductances

- AC Coupling

- Input-coupling capacitors are sometimes referred to as DC-blocking Capacitors
- Improved isolation between stages because the capacitors “block” DC current/voltages ($Z_c = 1/j\omega C \rightarrow \text{infinite impedance at } \omega = 0$)
- Impacts the low-frequency response

- Impact of Parasitics (Stray Inductances/Capacitances)

- Stray inductances/capacitances (often called “parasitics”) result from non-ideal properties of materials:
 - * Integrated circuits, chip packages, printed circuit boards, cables, ...

- High-frequency gain reduction from:
 - * Capacitors in parallel with the signal path
 - * Inductors in series with the signal path
- Computer-based simulations are used for complex models and circuits
- Half-Power Bandwidth
 - $P_o = (AV_{\text{inRMS}})^2/R_L \rightarrow P_o = P_{\text{max}}/2$ when $A = A_{\text{max}}/\sqrt{2}$
 - By convention, the frequencies f_H and f_L at which $P_o = P_{\text{max}}/2$ are referred to as half-power frequencies or -3db frequencies
 - * Note: $20 \log(A_{\text{max}}/\sqrt{2}) = 20 \log(A_{\text{max}}) - 20 \log(\sqrt{2}) = A_{\text{max(dB)}} - 3.01\text{dB}$
 - Amplifier bandwidth: $B = f_H - f_L$