

Lecture 5

Michael Brodskiy

Professor: M. Onabajo

September 18, 2024

- Finite Open-Loop Gain and Bandwidth
 - Assumptions during most previous examples
 - * Infinite A_{0OL} (subscript “0” indicates DC gain)
 - * Gain independence with respect to frequency (“flat gain”)
 - Open-loop gain of a typical (real) op-amp:
 - * Single-pole approximation (F_{BOL} = break frequency)
 - * High-frequency roll-off with -20dB/dec (single-pole approximation — for first order filters, can approximate $f_t = A_{0OL}f_{BOL}$)
 - * f_t = transition frequency (unity-gain)
- Mathematical Representation of Finite Gain/Bandwidth
 - A_{0OL} = DC gain, ω_+ = break frequency, ω_t = unity-gain frequency
 - Op-amp model with a transfer function of a single-pole low-pass filter:

$$A(\omega) = \frac{A_{0OL}}{1 + (j\omega/\omega_B)}, \quad |A(\omega)| = \frac{A_{0OL}}{\sqrt{1 + \left(\frac{\omega}{\omega_B}\right)^2}}$$

- Inverting Amplifier Analysis
 - High closed-loop gain (high R_2/R_1 ratio) reduces the closed-loop break frequency
- Closed-Loop Gain versus Break Frequency Trade-off
 - Fundamental gain-bandwidth (GBW) product limitation:

$$f_t = A_{0OL}f_{BOL} = A_{0CL}f_{BCL}$$

- When $f \gg f_B$:

$$|A(f)| \approx A_{0OL} \cdot \frac{f_B}{f} = \frac{f_t}{f}$$

- Closed-Loop: Gain Bandwidth $\propto f_{3dB}$

- When an op-amp is connected in a feedback configuration, the gain-bandwidth product (f_t) remains unchanged
- The 3dB frequency (break frequency) depends on feedback network components
- Gain-bandwidth product ($f_t = A_{0OL}f_{BOL}$)

- Large-Signal Operation: Voltage Swing

- Output voltage swing limitation
 - * The output voltage can only be in the following range:

$$V_{S-} + x < V_o < V_{S+} - x$$

- * The output limits should be specified in the manufacturers datasheet
- Clipping (saturation) occurs if the above condition is not met

- Linear Operating Range

- The input/output transfer characteristic of an op-amp (with a specified supply) voltage provide valuable information about large-signal operation

- Large-Signal Operation: Current Restrictions

- Op-amps have specified output current limits
- The op-amp must source/sink the current to/from load impedance (and feedback network elements)
- Careful: Small load or feedback resistors \rightarrow high I_o
- Clipping occurs when $I_o > I_{\text{limit}}$ would be required, but $I_o = I_{\text{limit}}$

- Finite Open-Loop Gain and Bandwidth

$$A(f) = \frac{A_{0OL}}{1 + j(f/f_{BOL})}$$

- Closed-Loop Impact of Finite Gain/Bandwidth

- * Inverting amplifier: $G = -\frac{R_2}{R_1}$
- * Non-inverting amplifier: $G = 1 + \frac{R_2}{R_1}$
- * For both cases: $f_{3dB} \approx \frac{f_t}{1+(R_2/R_1)}$

- Output Slew-Rate Limitation

$$\left| \frac{dv_o(t)}{dt} \right| \leq SR$$

- The magnitude of the output voltage's rate of change can not exceed the slew-rate (SR) specification of the op-amp
- Typical $10^5[\text{V/s}] < SR < 10^8[\text{V/s}]$
- Usually the SR is specified with load resistance conditions