

# Homework 12

Michael Brodskiy

Professor: M. Onabajo

December 3, 2024

1. (a)  $D = ABC + \overline{AB}$

We begin by constructing the table. First, we put in each combination of inputs. Given that there are 3 inputs, there should be  $2^3 = 8$  combinations:

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	0
1	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0
1	1	1	1

From here, we can draw the circuit as:

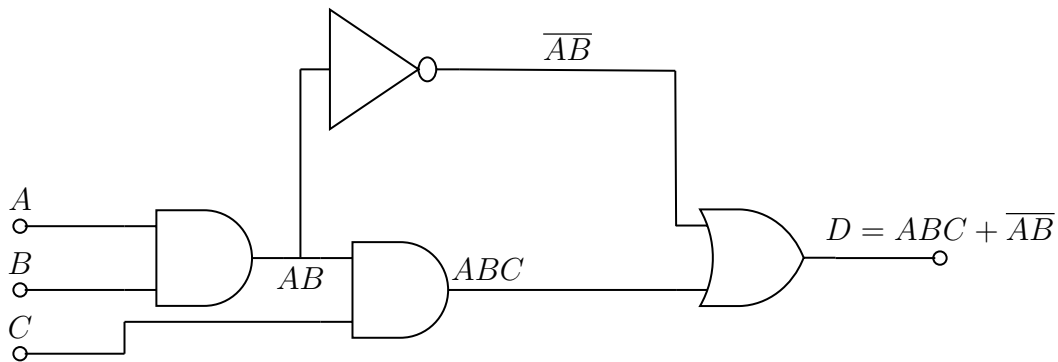


Figure 1: Logic Circuit for 1a

- (b)  $E = AB + \overline{A}BC + \overline{C}D$

Once again, we begin by analyzing each combination. Since there are 4 inputs, there are  $2^4 = 16$  possible inputs. This gives us:

A	B	C	D	E
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	1	0	0	0
1	0	0	0	0
0	0	1	1	0
0	1	0	1	1
1	0	0	1	1
0	1	1	0	0
1	0	1	0	1
1	1	0	0	1
0	1	1	1	0
1	0	1	1	1
1	1	1	0	1
1	1	0	1	1
1	1	1	1	1

This gives us the following circuit:

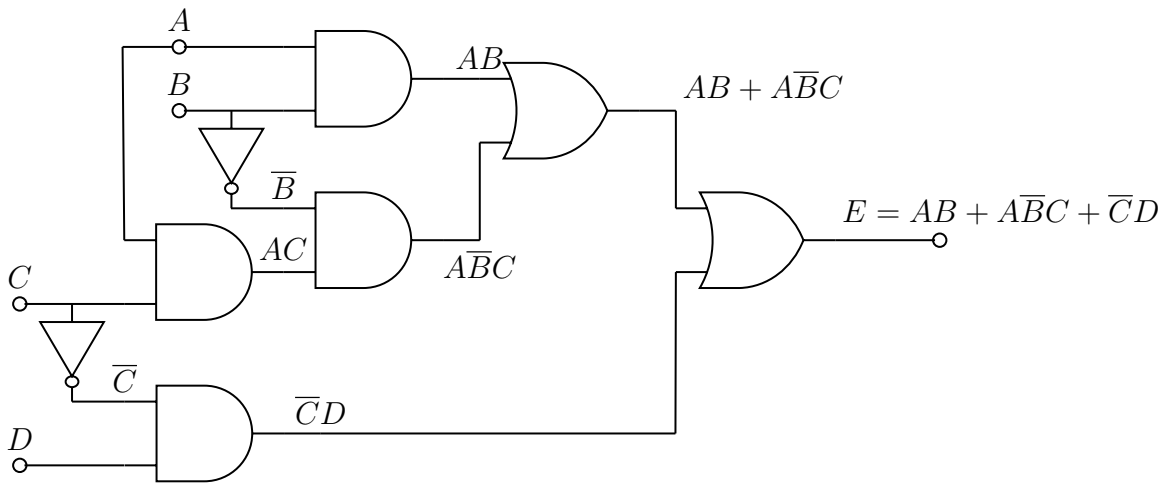


Figure 2: Logic Circuit for 1b

(c)  $Z = WX + \overline{(W + Y)}$

With three inputs, our table becomes:

W	X	Y	Z
0	0	0	1
0	0	1	0
0	1	0	1
1	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1
1	1	1	1

This gives the following circuit:

 


Figure 3: Logic Circuit for 1c

2. We can calculate the noise margins as:

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

This gives us:

$$NM_H = 4.5 - 3$$

$$NM_L = 1.5 - 1$$

And finally:

$$NM_L = .5[V] \quad \text{and} \quad NM_H = 1.5[V]$$

3. The switching times may be calculated using:

$$t_{PHL} = \frac{C_L V_{DD}}{\left(\frac{W}{L}\right)_n K P_n (V_{DD} - V_{ton})^2}$$

and

$$t_{PLH} = \frac{C_L V_{DD}}{\left(\frac{W}{L}\right)_p K P_p (V_{DD} - |V_{top}|)^2}$$

(a) For  $(W/L)_n = 3$  and  $(W/L)_p = 6$ , we get:

$$t_{PHL} = \frac{(2 \cdot 10^{-12})(5)}{(3)(50 \cdot 10^{-6})(5 - 1)^2}$$

$$t_{PLH} = \frac{(2 \cdot 10^{-12})(5)}{(6)(25 \cdot 10^{-6})(5 - | - 1 |)^2}$$

This results in:

$$\boxed{t_{PHL} = t_{PLH} = 4.166\bar{6}[\text{ns}]}$$

(b) For  $(W/L)_n = 3$  and  $(W/L)_p = 60$ , we get:

$$t_{PHL} = \frac{(2 \cdot 10^{-12})(5)}{(3)(50 \cdot 10^{-6})(5 - 1)^2}$$

$$t_{PLH} = \frac{(2 \cdot 10^{-12})(5)}{(60)(25 \cdot 10^{-6})(5 - | - 1 |)^2}$$

This results in:

$$\boxed{t_{PHL} = 4.166\bar{6}[\text{ns}] \quad \text{and} \quad t_{PLH} = .416\bar{6}[\text{ns}]}$$

(c) For  $(W/L)_n = 30$  and  $(W/L)_p = 6$ , we get:

$$t_{PHL} = \frac{(2 \cdot 10^{-12})(5)}{(30)(50 \cdot 10^{-6})(5 - 1)^2}$$

$$t_{PLH} = \frac{(2 \cdot 10^{-12})(5)}{(6)(25 \cdot 10^{-6})(5 - | - 1 |)^2}$$

This results in:

$$\boxed{t_{PHL} = .416\bar{6}[\text{ns}] \quad \text{and} \quad t_{PLH} = 4.166\bar{6}[\text{ns}]}$$

4. (a) Given that both transistors are expected to be in saturation, we may use our formulas to equate:

$$I_n = \left(\frac{W}{L}\right)_n \left(\frac{K P_n}{2}\right) (V_{in} - V_{ton})^2 (1 + \lambda V_{DD}/2)$$

$$I_p = \left(\frac{W}{L}\right)_p \left(\frac{K P_p}{2}\right) (V_{in} - V_{DD} - |V_{top}|)^2 (1 + \lambda V_{DD}/2)$$

This allows us to rearrange and get:

$$\frac{W_p}{W_n} = \left[ \frac{V_{in} - V_{ton}}{V_{in} - V_{DD} - |V_{top}|} \right]^2 \left( \frac{KP_n}{KP_p} \right)$$

We insert known values (and take the input as half the supply voltage) to get:

$$\frac{W_p}{W_n} = \left[ \frac{.6 - .3}{.6 - 1.2 - |-.4|} \right]^2 \left( \frac{90}{30} \right)$$

Evaluation, we find:

$$\boxed{\frac{W_p}{W_n} = .27}$$

(b) Taking one of our current equations from before, we get:

$$I_n = \left( \frac{W}{L} \right)_n \left( \frac{KP_n}{2} \right) (V_{in} - V_{ton})^2 (1 + \lambda V_{DD}/2)$$

We substitute the given values to get:

$$.05 \cdot 10^{-3} = \left( \frac{W_n}{.12 \cdot 10^{-6}} \right) \left( \frac{90 \cdot 10^{-6}}{2} \right) (.6 - .3)^2 (1 + .05(.6))$$

Evaluating, we find:

$$\boxed{W_n = 1.4383[\mu\text{m}]}$$

Using our ratio, we obtain:

$$W_p = .27W_n$$

$$W_p = .27(1.4383)$$

$$\boxed{W_p = .38835[\mu\text{m}]}$$

(c) The above results allow us to obtain the following DC transfer characteristics:

 


Figure 4: DC Transfer Characteristics of CMOS Inverter

5. Power dissipation of a CMOS is given by:

$$P_d = C f V_{DD}^2$$

Substituting our known values gives us:

$$P_d = (100 \cdot 10^{-15})(100 \cdot 10^6)(3)^2$$

Thus we get:

$$P_d = 9 \cdot 10^{-5} [\text{W}]$$

Note that there is no dissipation when  $V_{DD} = 0[\text{V}]$

6. The pull-up network may be drawn as:

 


Figure 5: Corresponding Pull-Up Network

The pull-down network then becomes:

 


Figure 6: Corresponding Pull-Down Network

We combine the two to form the full network:

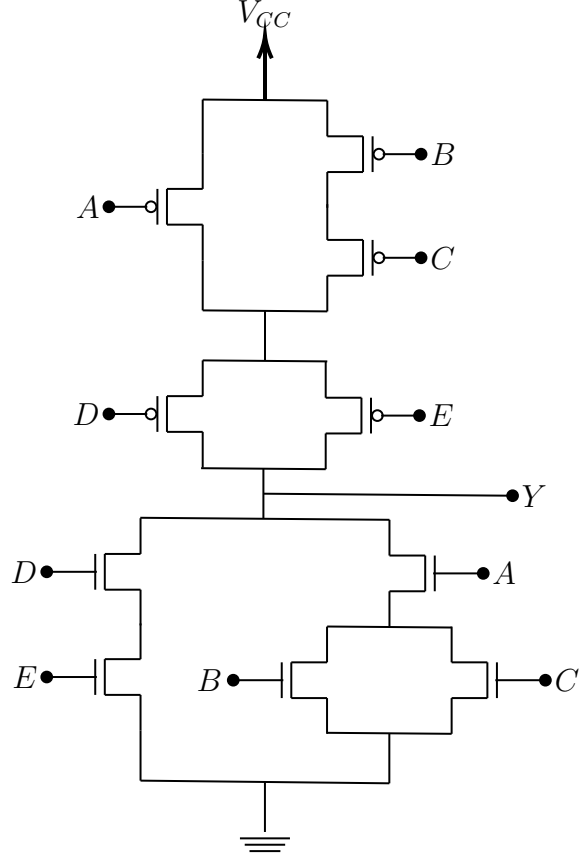


Figure 7: Corresponding Network

We may observe that 10 transistors are needed, 5 for the pull-up and 5 for the pull-down networks.

7. From the provided diagram, and a value for PMOS resistance,  $R_p$ , we may observe:

$$R_{M1} = R_p \quad \text{and} \quad R_{M2} + R_{M3} = R_p$$

Furthermore, since we are using the same PMOS transistors, we may write:

$$R_{M2} = R_{M3} \implies 2R_{M2} = 2R_{M3} = R_p$$

This means that:

$$\boxed{\left(\frac{W}{L}\right)_{M1} = \left(\frac{W}{L}\right)_p}$$

$$\boxed{\left(\frac{W}{L}\right)_{M2} = \left(\frac{W}{L}\right)_{M3} = 2\left(\frac{W}{L}\right)_p}$$



We can see that, for the pull-down branch, we have:

$$R_{M4} + R_{M5} = R_n \quad \text{and} \quad R_{M4} = R_{M5}$$

This gets us:

$$\boxed{\left(\frac{W}{L}\right)_{M4} = \left(\frac{W}{L}\right)_{M5} = 2\left(\frac{W}{L}\right)_n}$$

We can see that the sixth transistor is equivalent to this, and we get our last value as:

$$\boxed{\left(\frac{W}{L}\right)_{M6} = 2\left(\frac{W}{L}\right)_n}$$